

MyRISC

A VHDL implementation of a 16-bit RISC processor

Final Project for ENGS 128: Advanced Digital Systems Design

Professor Hansen

BRETT R. NICHOLAS

MATTHEW T. METZLER

Table of Contents

Project Introduction	4
Overview	4
High-Level Overview	4
Top-Level Block Diagram	4
Functionality	5
Control Unit	5
Datapath	5
Instruction Buffer	5
General Purpose RAM (BRAM)	5
Instruction RAM (XRAM)	5
Serial Receiver & Transmitter	5
Debouncer & Monopulser	6
7-segment Display	6
Top-level Port Descriptions	6
Functional Description	7
Modes of operation	7
Program Mode	7
Execution Mode	7
Instructions	8
Instruction Set	8
Instruction Format	8
Simulation Waveforms	9
Program Mode	9
Execution Mode	11
Hardware Implementation	19
Utilization Summary	19
Timing Summary	20
Component Architecture	22
Control Unit	22
Functionality	22
FSM	22
Datapath	22
Functionality	22
RTL Schematic	23
Instruction Buffer	23
Functionality	23
FSM	24
General Purpose Memory (BRAM)	24
Functionality	24
Instruction Memory (XRAM)	25
Functionality	25
Error Generation	25

Functionality.....	25
FSM.....	25
Results and Discussion	26
Appendix	28
Appendix A: VHDL Style Conventions.....	29
Appendix B: VHDL Source Listings.....	30
Top Level	30
Controller	34
Datapath.....	39
Instruction Buffer	41
Error Generator	44
Serial Receiver	46
Serial Transmitter	48
Monopulser	50
Debouncer	51
7-segment display	52
Appendix C: Control Unit FSM Diagram	54


Project Introduction

Overview

In the project we have designed a simple reduced instruction set architecture (RISC) microprocessor implemented on a field-programmable gate array (FPGA). This processor executes 16-bit instructions stored in instruction random access memory (RAM) one at a time using 16 general purpose registers and a general purpose block RAM. We began by storing our instructions in read-only memory, but after completing the processing functionality of the design, we decided to allow user interaction with the processor by allowing real-time programming through serial communication with the board. The user can type instructions in hexadecimal format into *PuTTY* to program the board, and then step through program execution one instruction at a time using a push button.

High-Level Overview

Top-Level Block Diagram

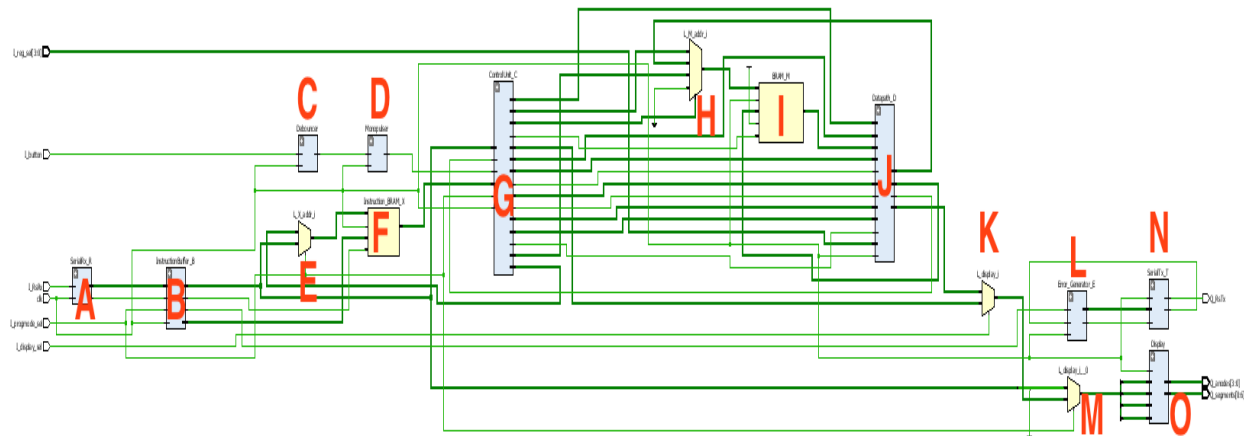

Key	Component	Key	Component
A	Serial Receiver	I	General Purpose RAM
B	Instruction Buffer	J	Datapath
C	Debouncer	K	7-segment display MUX1
D	Monopulser	L	Error Generator
E	Instruction RAM Address MUX	M	7-segment display MUX2
F	Instruction RAM	N	Serial Transmitter
G	Control Unit	O	7-segment Display
H	General Purpose RAM Address MUX		

Functionality

Control Unit

The control unit consists of an FSM controller, four special purpose registers, and a small amount of dedicated combinational logic. The FSM controller guides the processor through the various generic states of program execution – *Fetch, Decode, Load Operands, Execute, Store* – and also handles other component's access to memory. The processor utilizes a "Harvard Architecture", which means instructions are stored in a separate memory from the general purpose memory, so the controller must handle simultaneous communication with both memories. The four special purpose registers contained in the control unit are the Program Counter (PC), the Instruction Register (IR), the Link Register (LR), and the Stack Pointer (SP). A more detailed description of controller functionality is provided in the Component Architecture section.

Datapath

The Datapath consists of a 16x16-bit multipurpose register file with two pipelined outputs, an Arithmetic Logic Unit (ALU), and various input and output multiplexors. The controller is responsible for selecting from the register file the appropriate registers from which to read and write. Any two of the 16 registers can be multiplexed into the two designated read pipeline registers (Preg and Qreg), and any one of the 16 registers can be written to from a number of different sources as designated by the controller. A more detailed description of Datapath functionality is provided in the Component Architecture section.

Instruction Buffer

The instruction buffer is a state machine-controlled character buffer that allows for the user to program the instruction memory (XRAM) over USART. The instruction buffer shifts each received character from the serial receiver into the buffer until a carriage return or error is detected. When a valid instruction is fully buffered, it is then written to instruction memory, and the buffer is ready to accept the next command. When programming is complete, the buffer stores the memory address of the last instruction so that the processor can halt execution after the final instruction. A more detailed description of the Instruction Buffer functionality is provided in the Component Architecture section.

General Purpose RAM (BRAM)

For general purpose memory, the processor employs a single-port read/write-enable 18k BRAM, instantiated as a Xilinx IP core using the Block Memory Generator. Memory access is handled by the control unit. A more detailed description of BRAM functionality is provided in the Component Architecture section.

Instruction RAM (XRAM)

For instruction memory, the processor employs another single-port read/write-enable 18k BRAM, instantiated as a Xilinx IP core using the Block Memory Generator. Memory is programmable by the user over USART, and access is shared by the control unit and the Instruction Buffer. A more detailed description of the XRAM functionality is provided in the Component Architecture section.

Serial Receiver & Transmitter

These pre-built components interact with the RS-232 serial port for serial communication between the board and the user.

Debouncer & Monopulser

The debouncer uses a counter and output register to filter out electrical noise during push button operation. The debounced signal is then fed into a monopulser that creates a one clock-width tick on any rising edge of the signal.

7-segment Display

The display driver controls the four 7-segment displays on the board. It does this by cycling through the four anodes with the corresponding 4-bit vector.

Top-level Port Descriptions

Port	Type	Peripheral Connectivity	Description
clk	std_logic		100 MHz system clock
I_RsRx	std_logic	USB-RS232 (pkg pin B18)	Serial data in
I_progmodesel	std_logic	Switch SW0 (pkg pin V17)	Allows user to toggle between program mode and execute mode
I_button	std_logic	Center board button BTNC (pkg pin U18)	Allows user to step through program execution, one instruction at a time
I_reg_sel	std_logic_vector (3 downto 0)	Switches SW15 down to SW12 (pkg pins R2, T1, U1, W2)	Allows user to select which register's contents are displayed on the 7-segment LED display
Q_RsTx	std_logic	USB-RS232 (pkg pin A18)	Serial data out
Q_segments	std_logic_vector (7 downto 0)	7-segment display	7-segment LED controls
Q_anodes	std_logic_vector (3 downto 0)	7-segment display	7-segment LED controls

Functional Description

Modes of operation


The processor can be operated in two modes: *program* mode and *execution* mode. The user can toggle between these two modes using a slide switch. *Program* mode, accessed by setting **SW0** to **HIGH**, allows users to enter instructions over USART which are then stored in instruction memory when the mode is changed. *Execution* mode, entered by setting **SW0** to **LOW**, waits for the user to press the center button (**BTNC**), upon which it will load the next instruction into the instruction register, execute the instruction, and then either wait for the next button press to continue or terminate execution when the last instruction is reached.

Program Mode

In the *program* mode the user enters processor instructions into *PuTTY* to be transmitted over the serial interface on the board. These commands, entered as four-character hexadecimal words followed by a carriage return (CR), are converted into instructions and saved to the instruction memory. The 7-segment display on the board displays which address in the instruction memory is currently being written to. The processor returns an "ERROR" message over the serial interface when the entered command word does not match the format specified below, and the command is ignored.

Execution Mode

In *execution* mode the user can step through the instructions using a pushbutton on the board. The user can use an array of switch slides to control the data shown on the 7-segment LED displays. The **SW1** switch toggles between displaying the program counter and the register file. When looking at the register file, four separate switch slides designate the binary address of the register the user wants to look at. While looking at the program counter on the display, the instruction held in that spot in memory is not executed until the user presses the pushbutton. The user can continue executing instructions until all the instructions read in the previous *program* mode have been performed, after which the processor idles until the user returns **SW0** to **LOW** to enter new commands.

 

Instructions

Instruction Set

Command	Description	Opcode		Operation
NOP	No operation	0000	x"0"	N/A
LDR	Load direct	0001	x"1"	$R_a \leftarrow M[d]$
STR	Store direct	0010	x"2"	$M[d] \leftarrow R_a$
MOV	Move	0011	x"3"	$R_a \leftarrow R_b$
LDC	Load constant	0100	x"4"	$R_a \leftarrow d$
ADD	Add	0101	x"5"	$R_a \leftarrow R_b + R_c$
SUB	Subtract	0110	x"6"	$R_a \leftarrow R_b - R_c$
BZ	Branch if zero	0111	x"7"	if($R_a = 0$) then $PC \leftarrow PC + d + 1$
BD	Branch direct	1000	x"8"	$PC \leftarrow d$
BL	Branch with link	1001	x"9"	$LR \leftarrow PC$ and $PC \leftarrow d$
LIN	Load indirect	1010	x"a"	$R_a \leftarrow M[R_c]$
SIN	Store indirect	1011	x"b"	$M[R_c] \leftarrow R_b$
PSH	Push registers to stack	1100	x"c"	Push(v); v is one-hot register selection vector 'PSH 010101010101' pushes r0, r2, r4, r6, r8, r10 onto stack
POP	Pop registers off stack	1101	x"d"	Pop(v); v is one-hot register selection vector 'POP 010101010101' pops r0, r2, r4, r6, r8, r10 from stack, assuming registers were pushed using the same order

Instruction Format


3 instruction types:

(15 downto 12)	(11 downto 8)	(7 downto 4)	(3 downto 0)
< Opcode >	< R _a >	< R _b >	< R _c >
	< R _a >	< d >	
	< Register Selection Vector >		


Simulation Waveforms

Program Mode


1: Programming XRAM

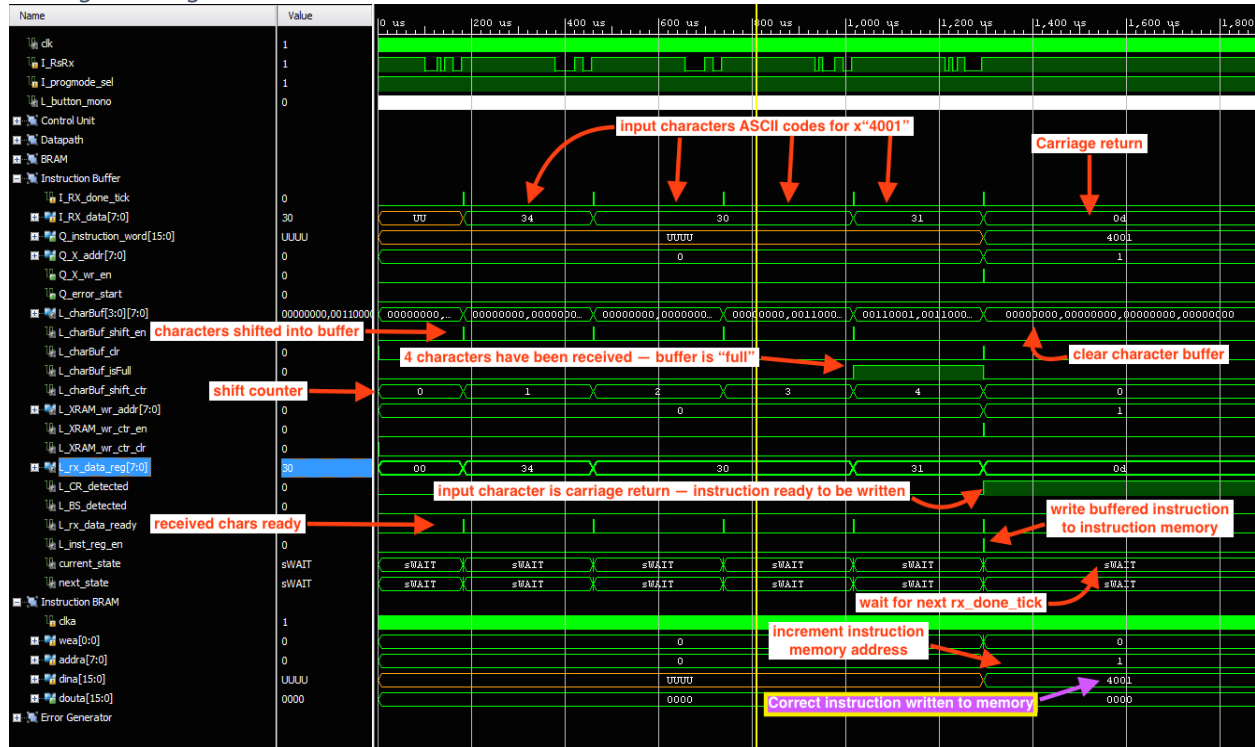


2: Character Buffering

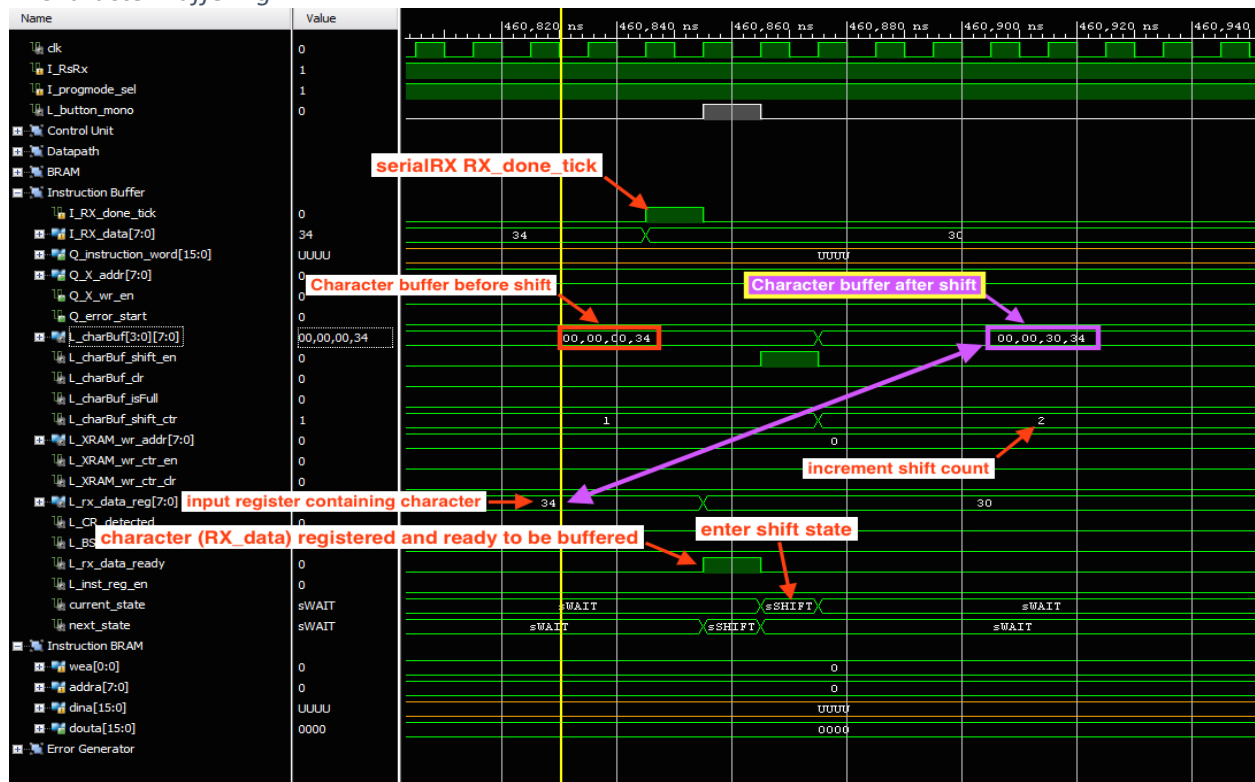

3: Programming Error Detection

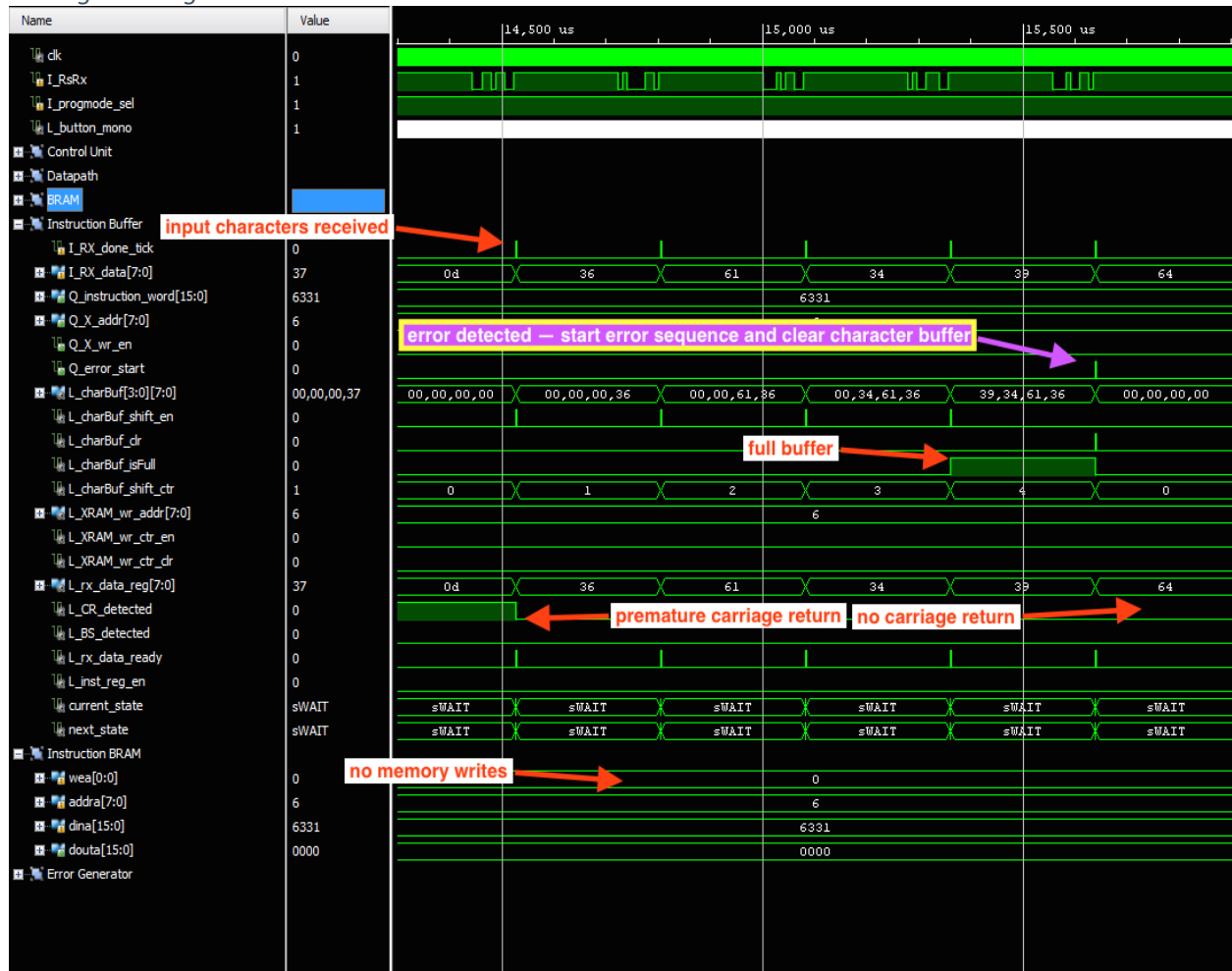


4: Error Message Transmission

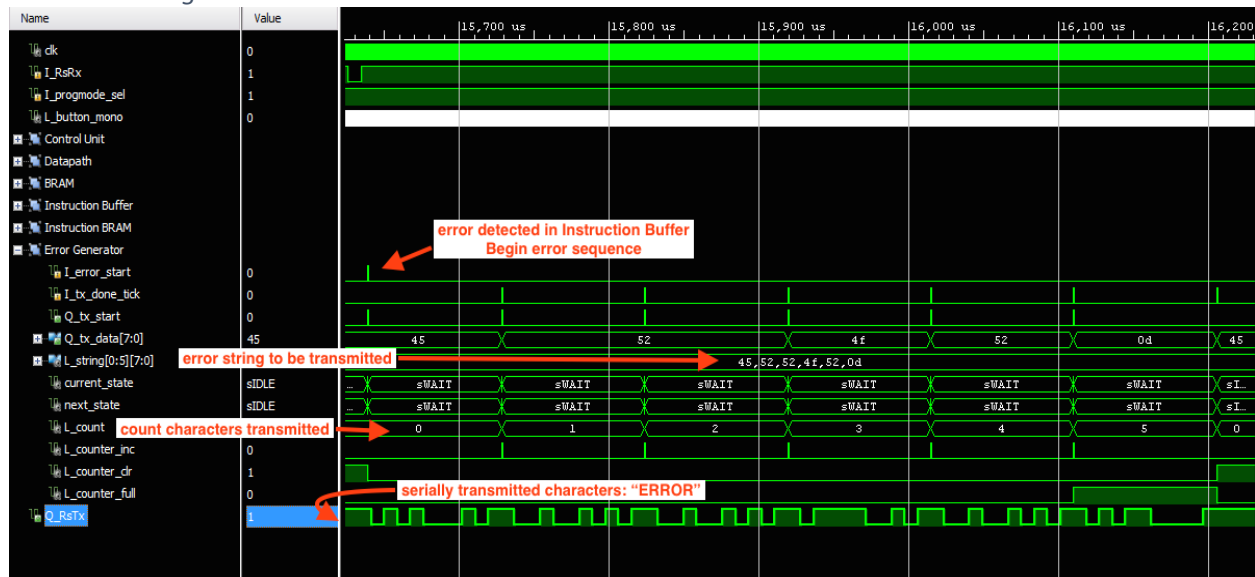


Execution Mode


5: Load Direct

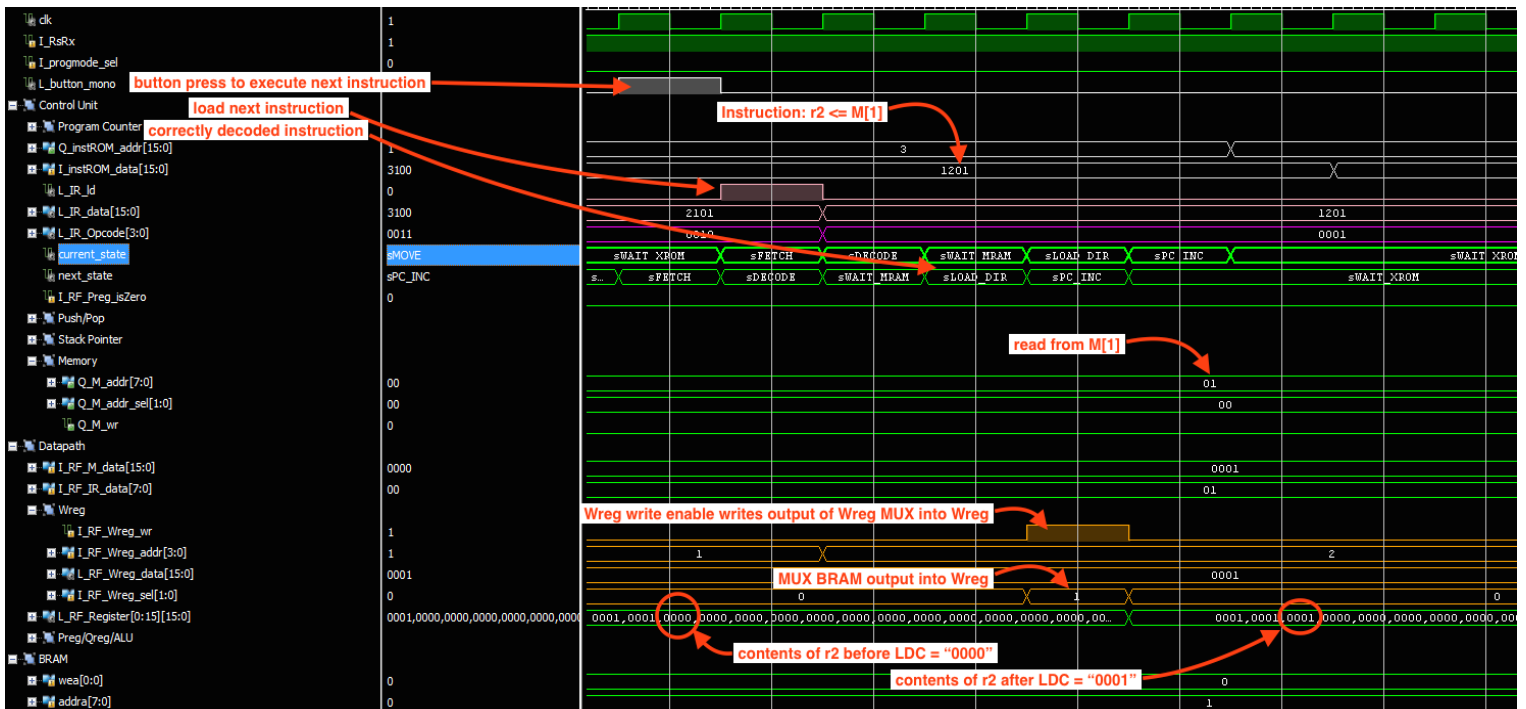


6: Store Direct

 


7: Move

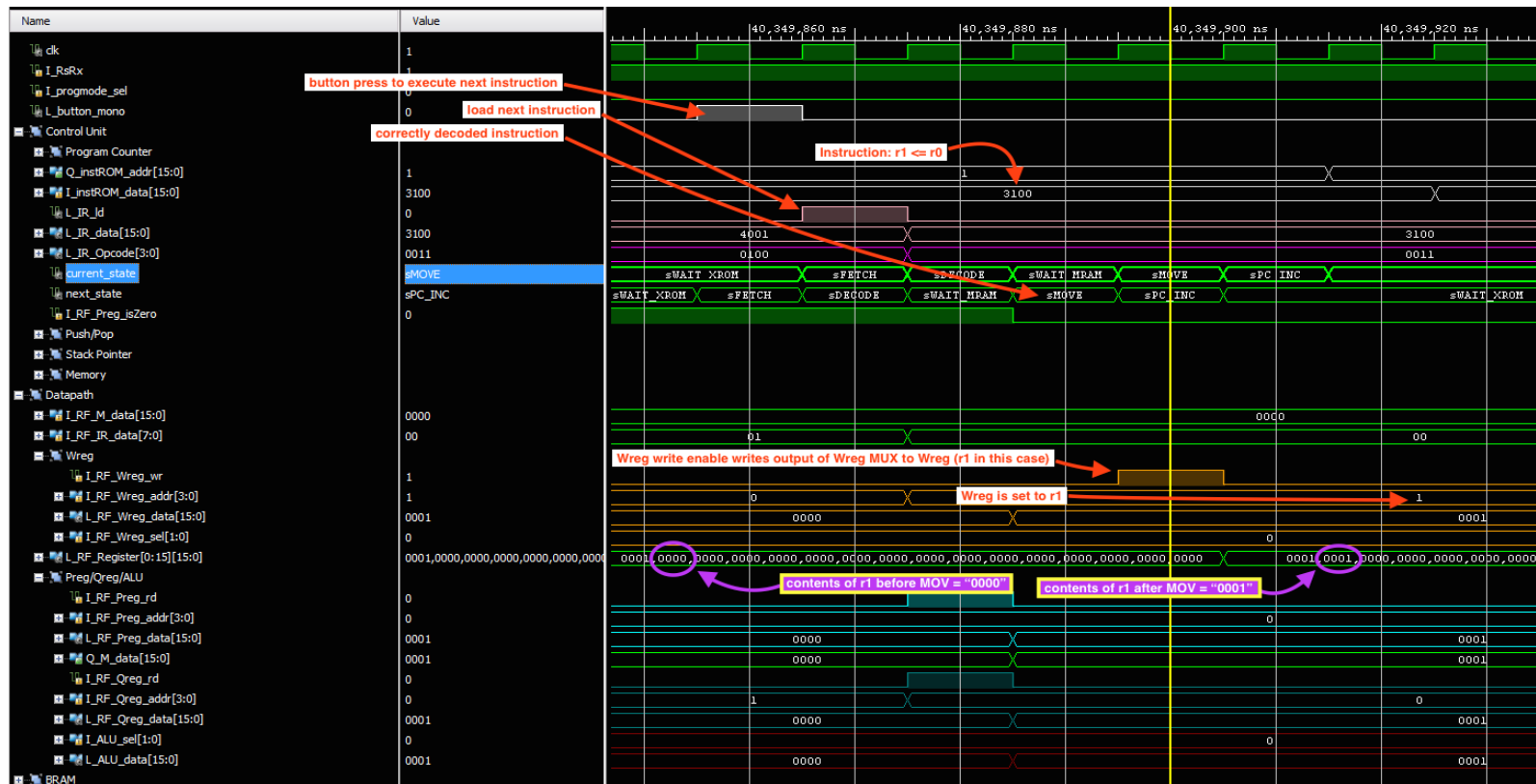


8: Load Constant

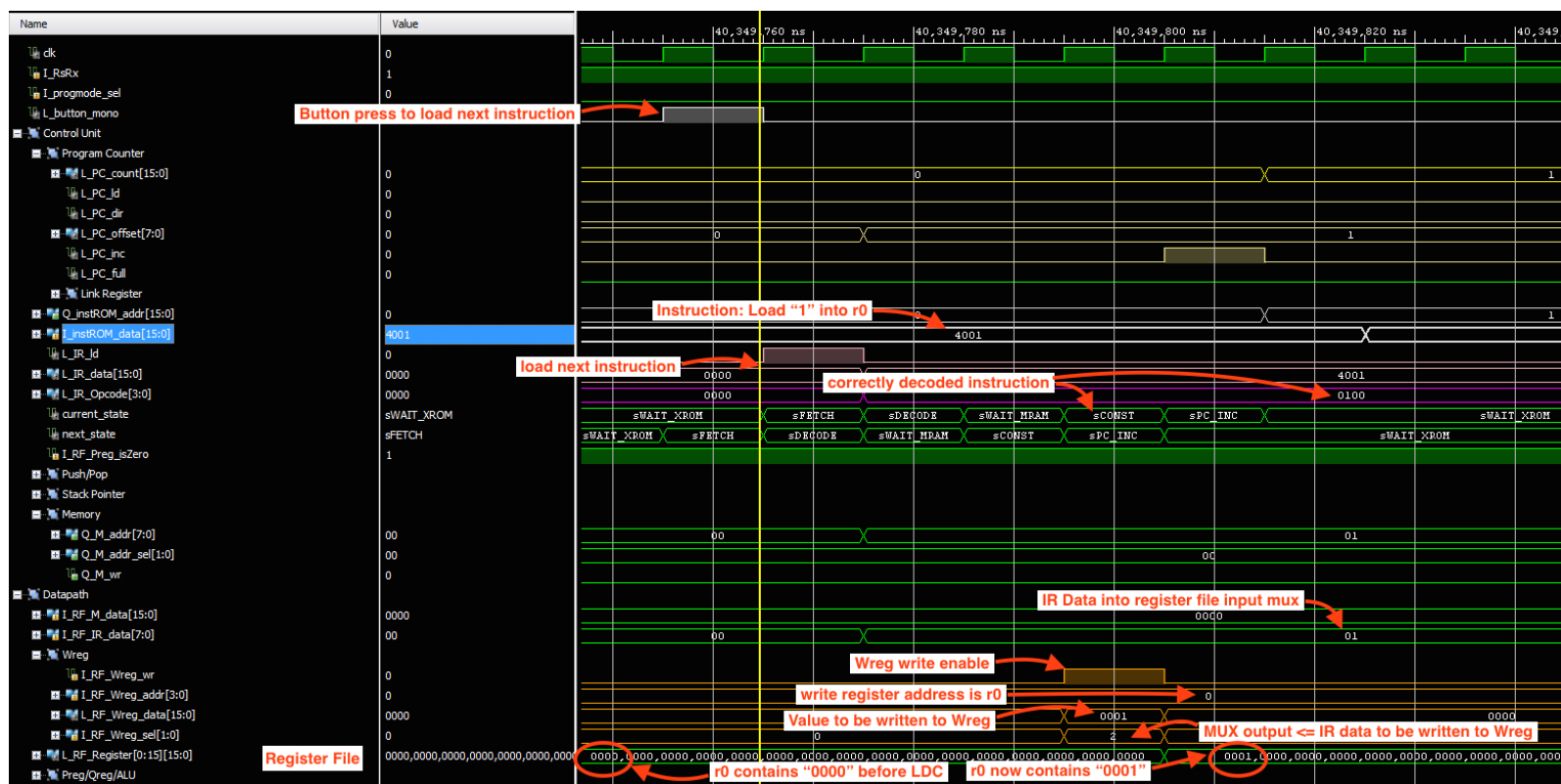


9: Add

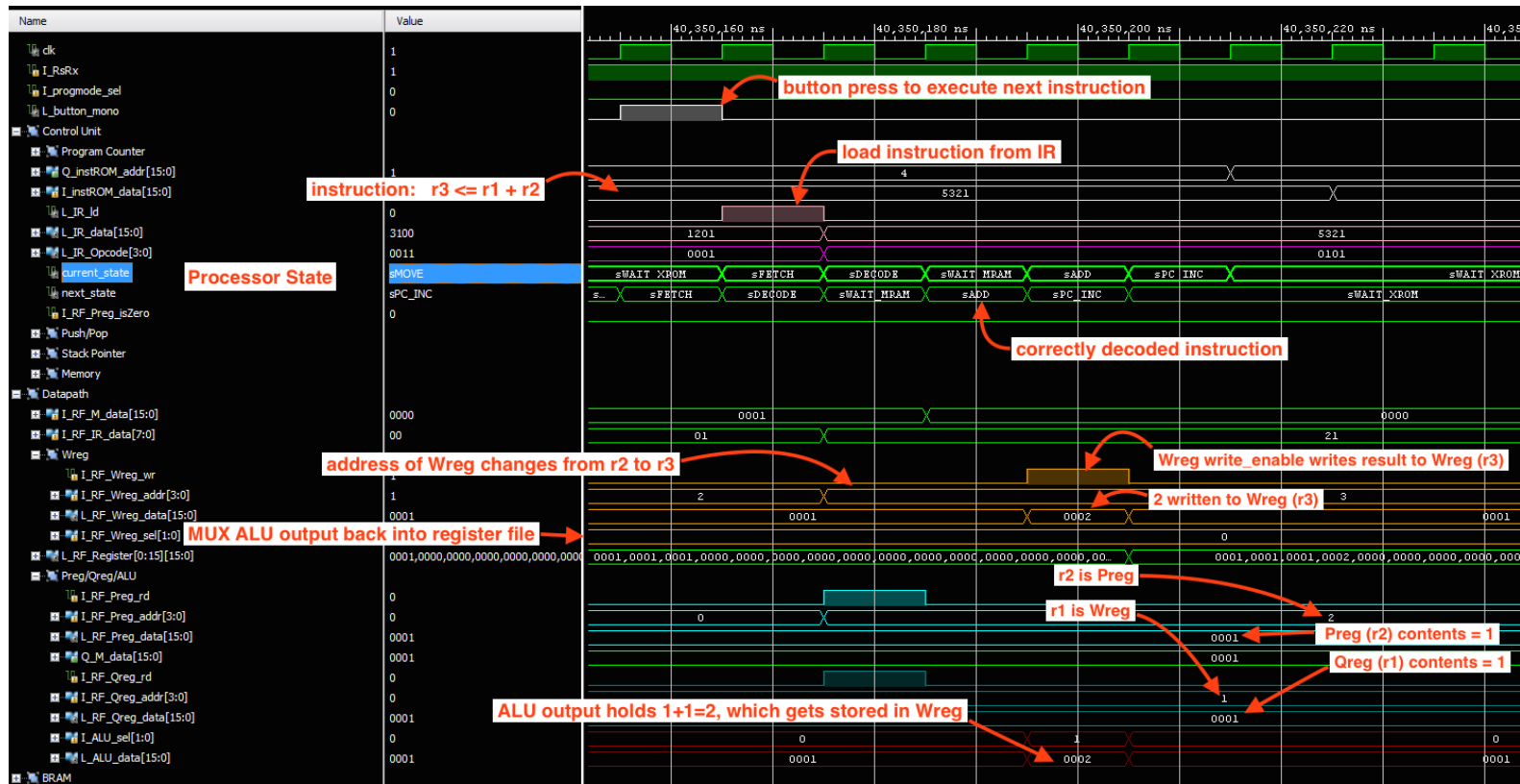


10: Subtract

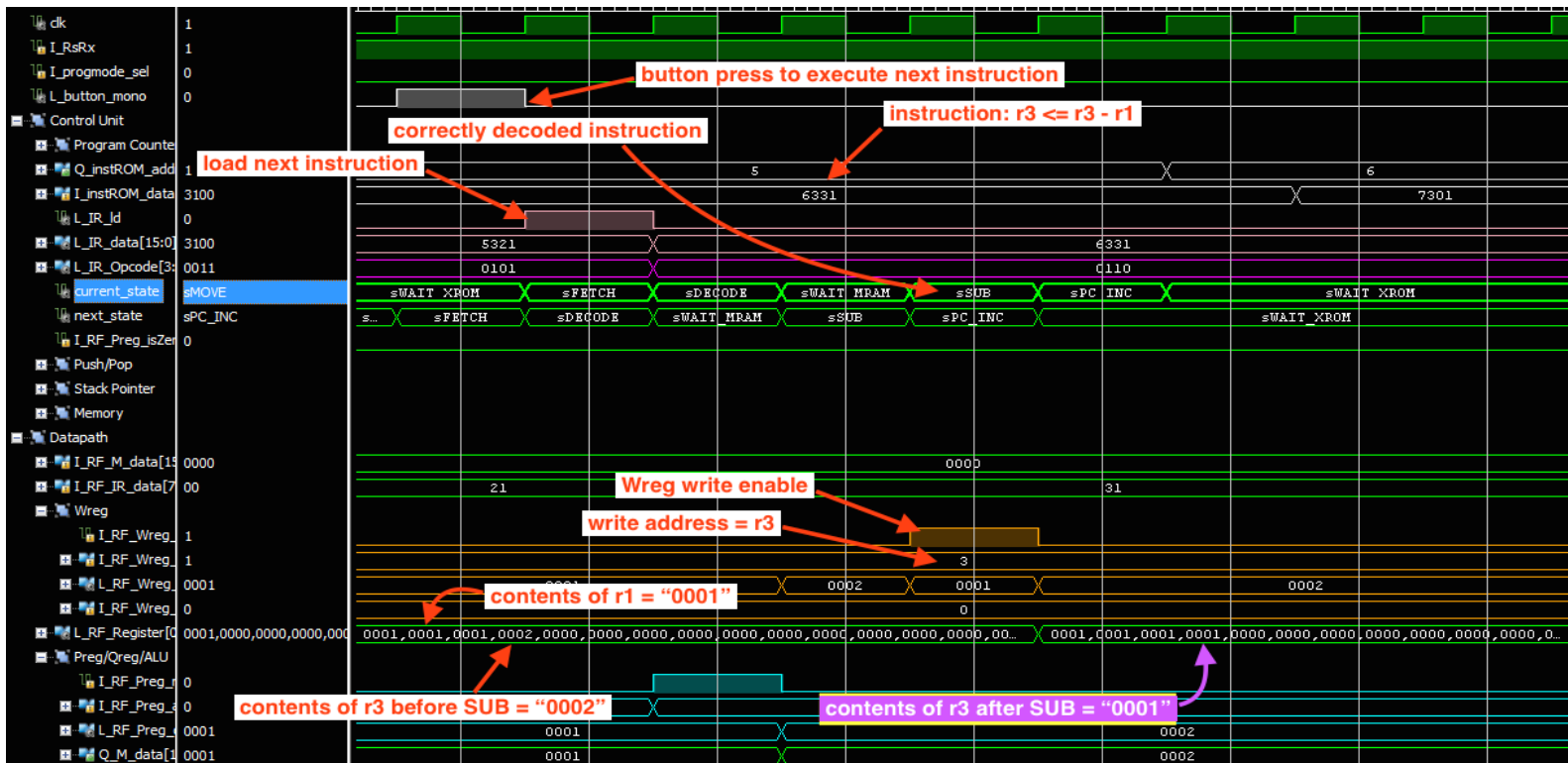


11: Branch if Zero (Successful branch)

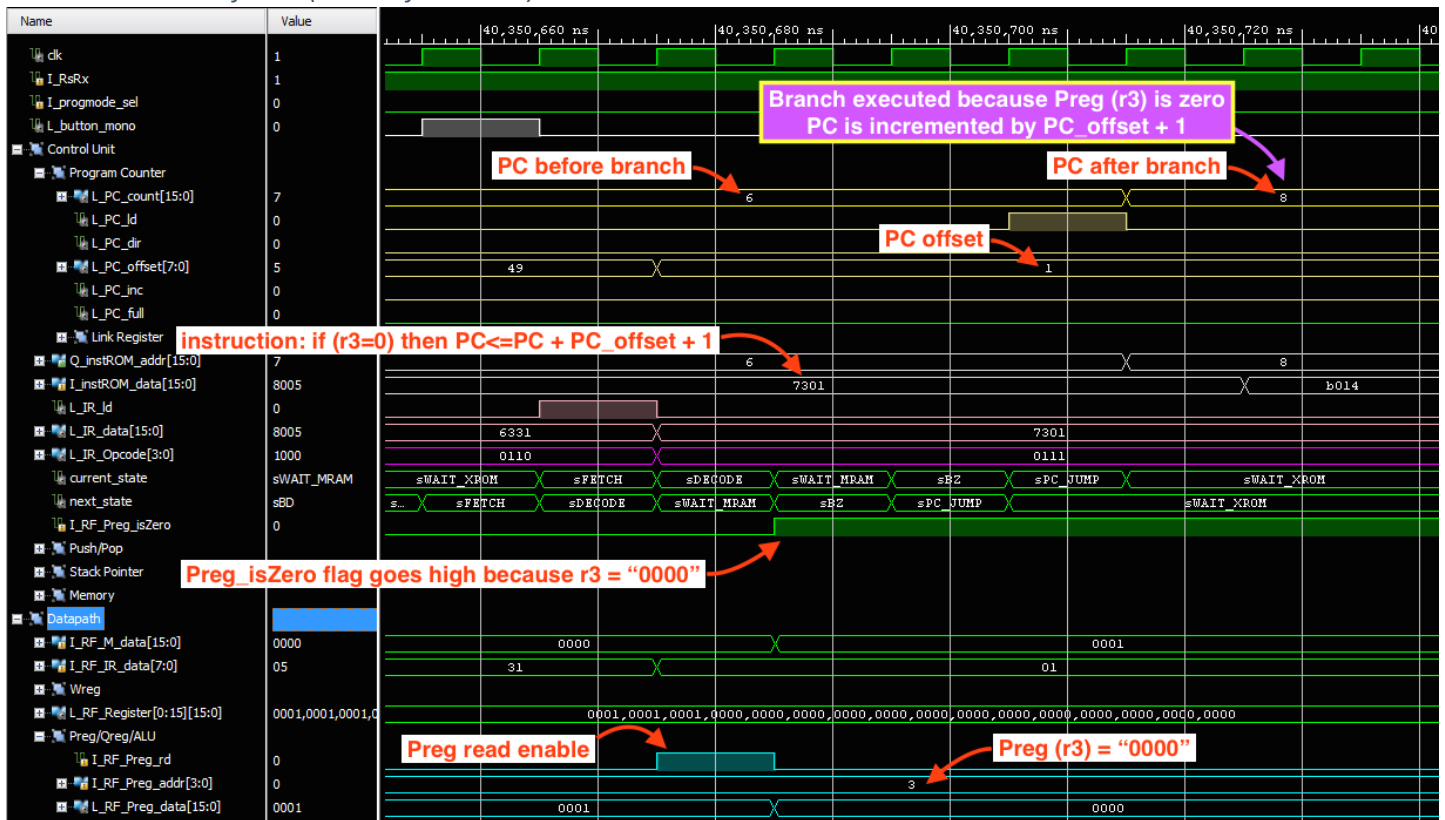


12: Branch if Zero (Failed Attempt)

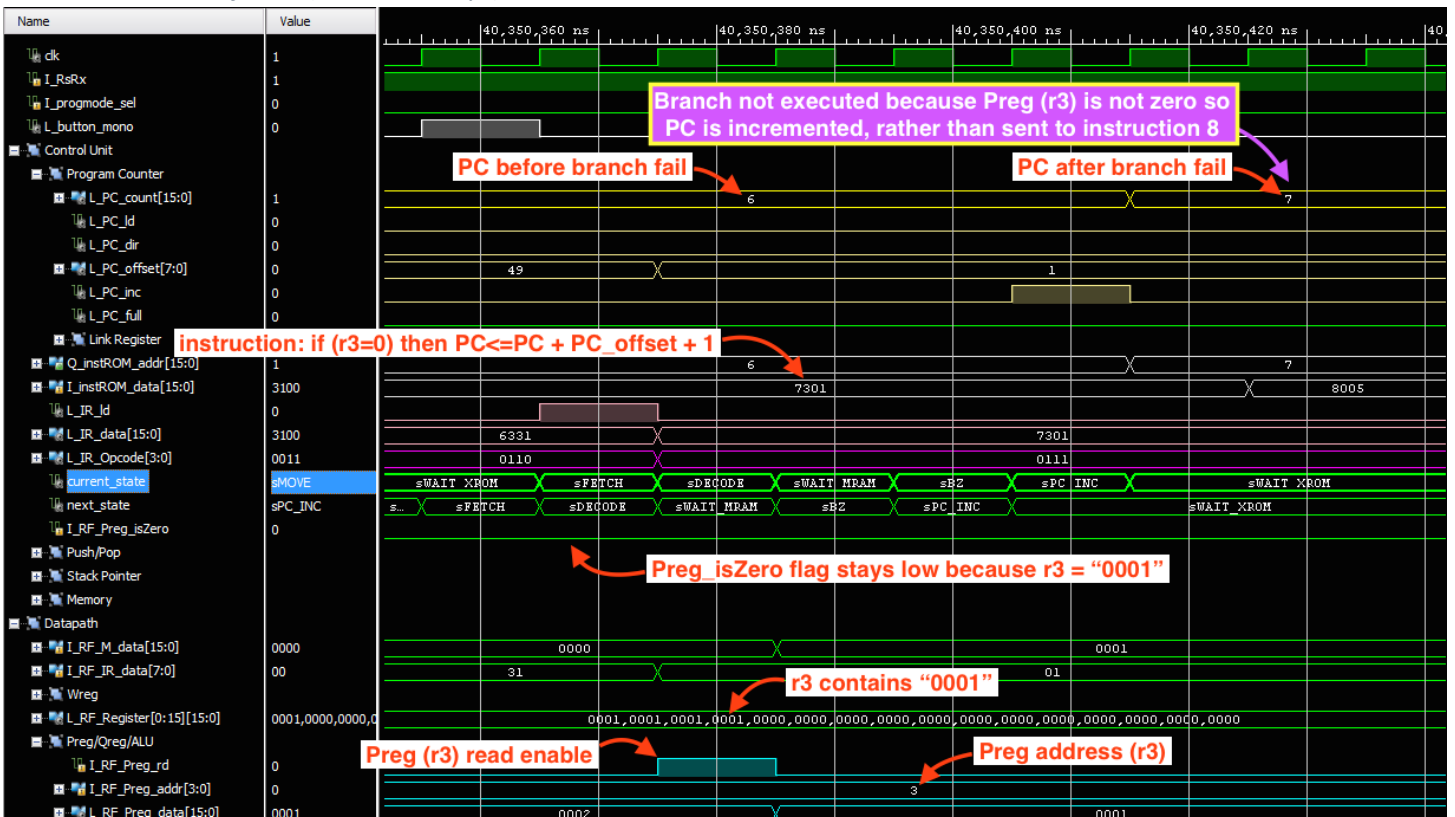


13: Branch Direct

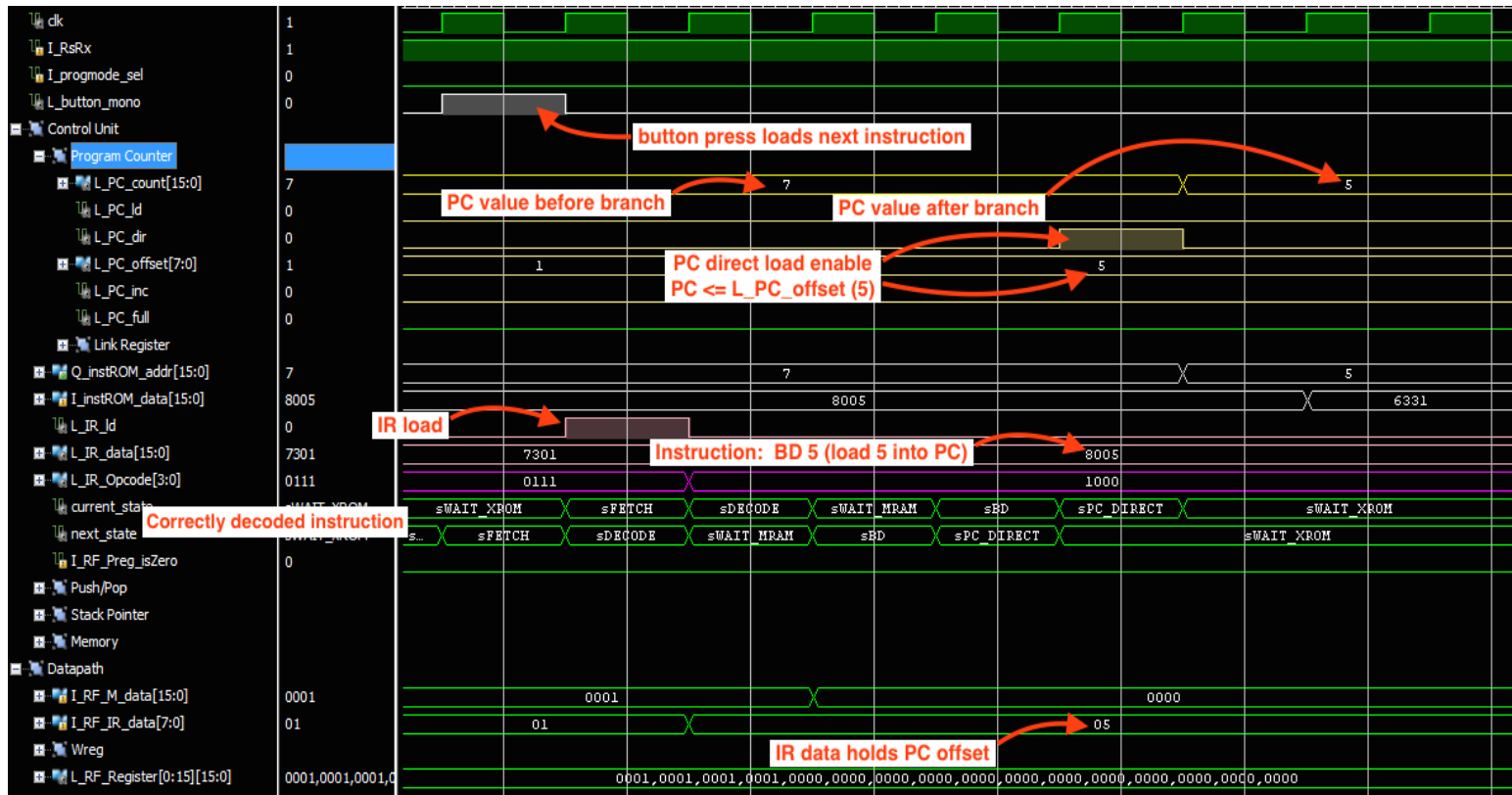


14: Branch with Link

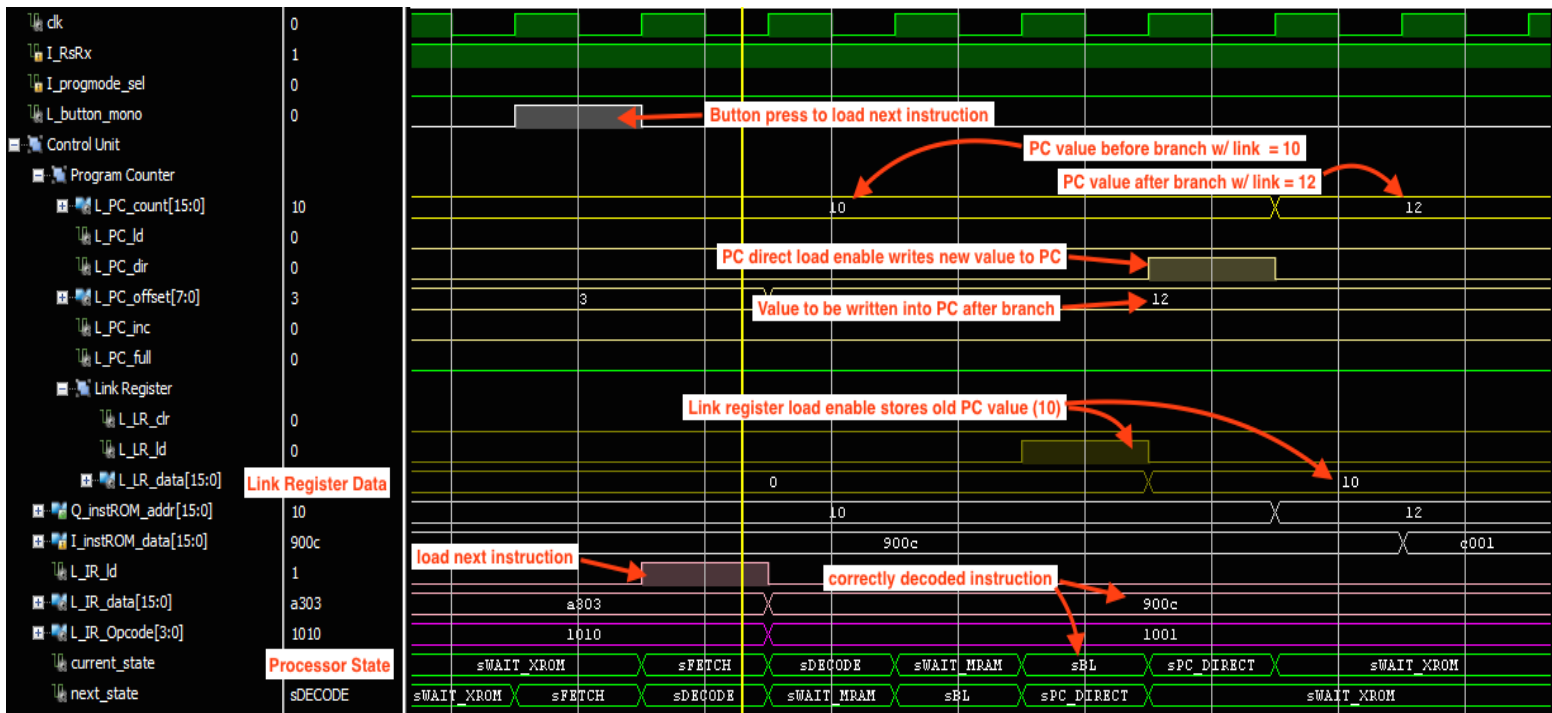


15: Load Indirect

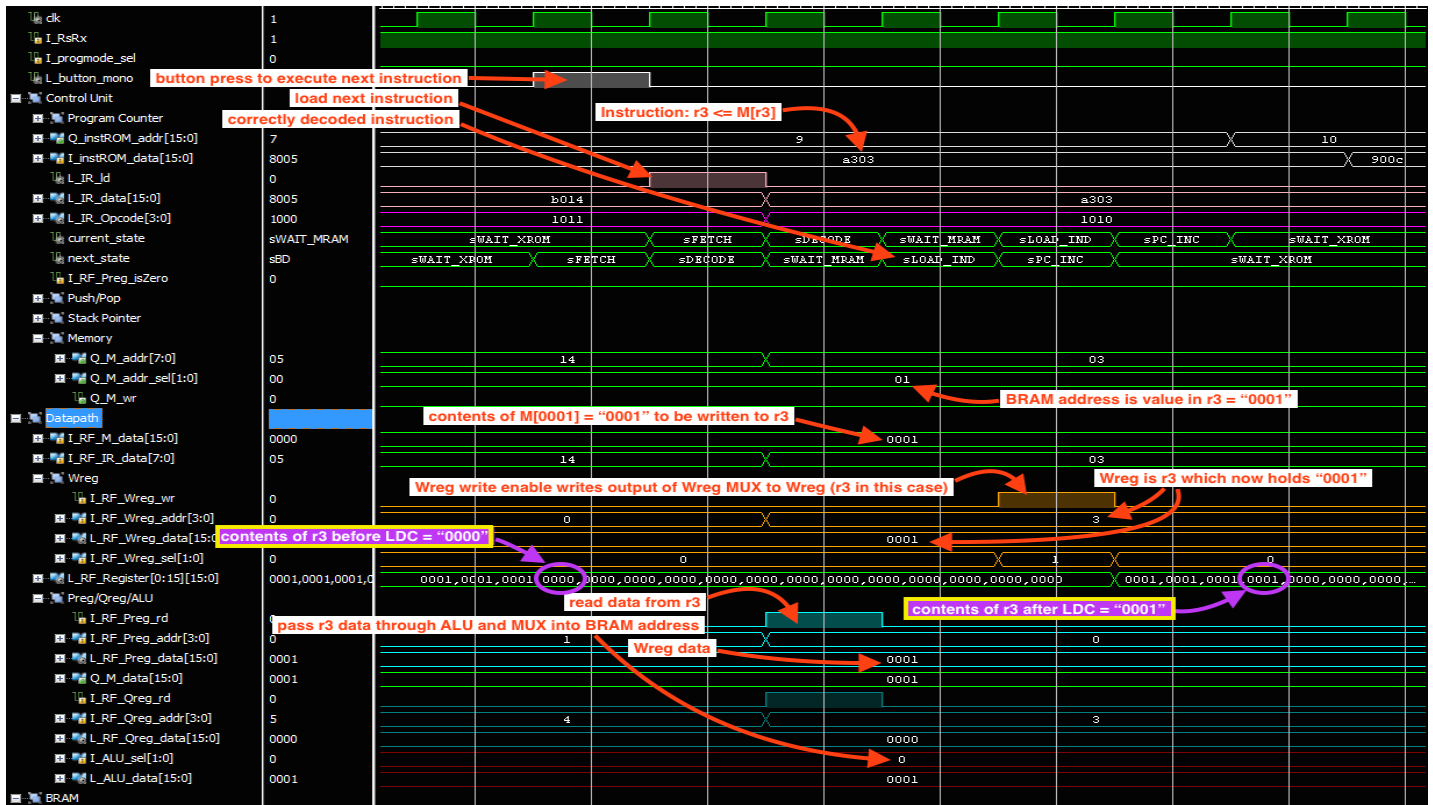


16: Store Indirect

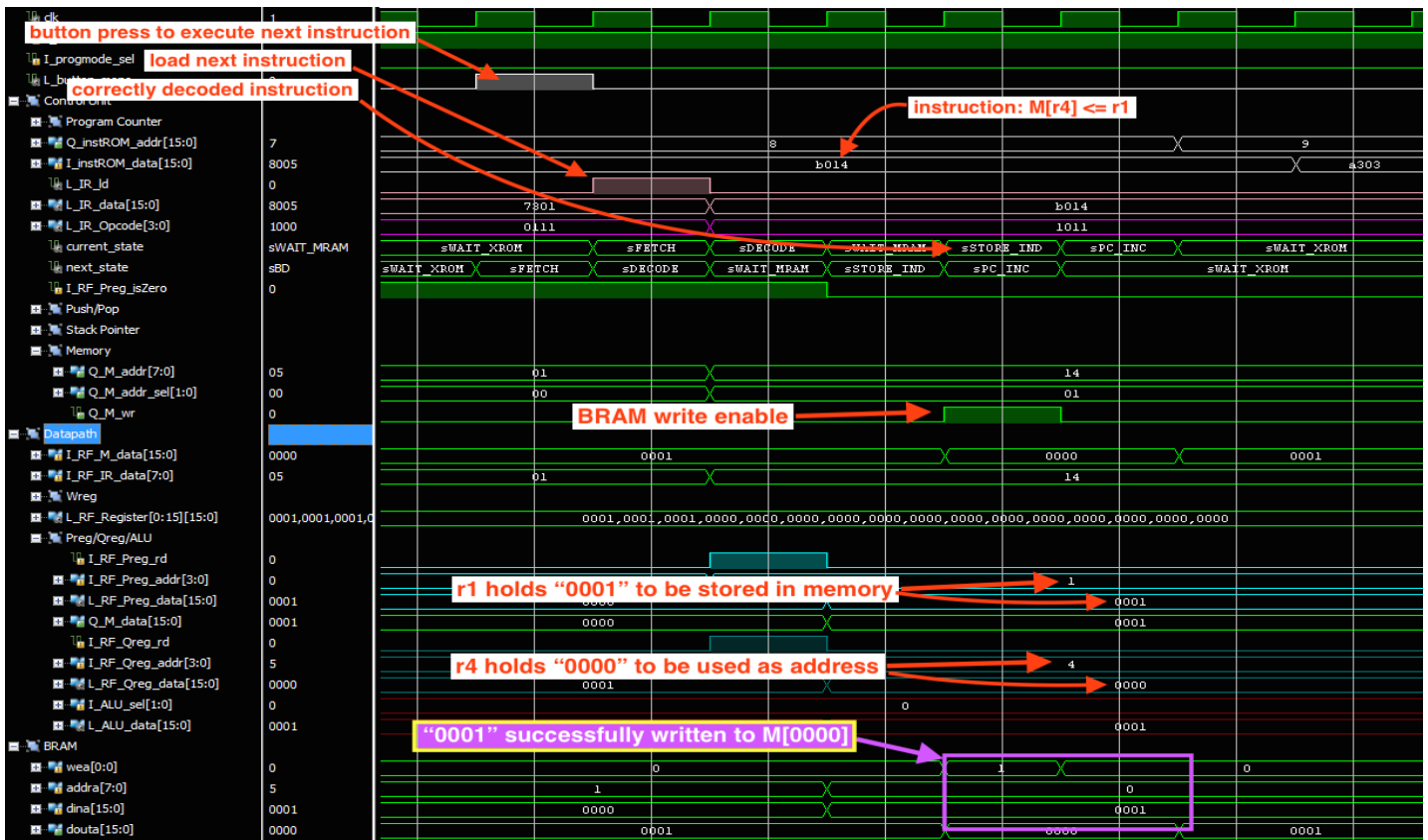


17: Push

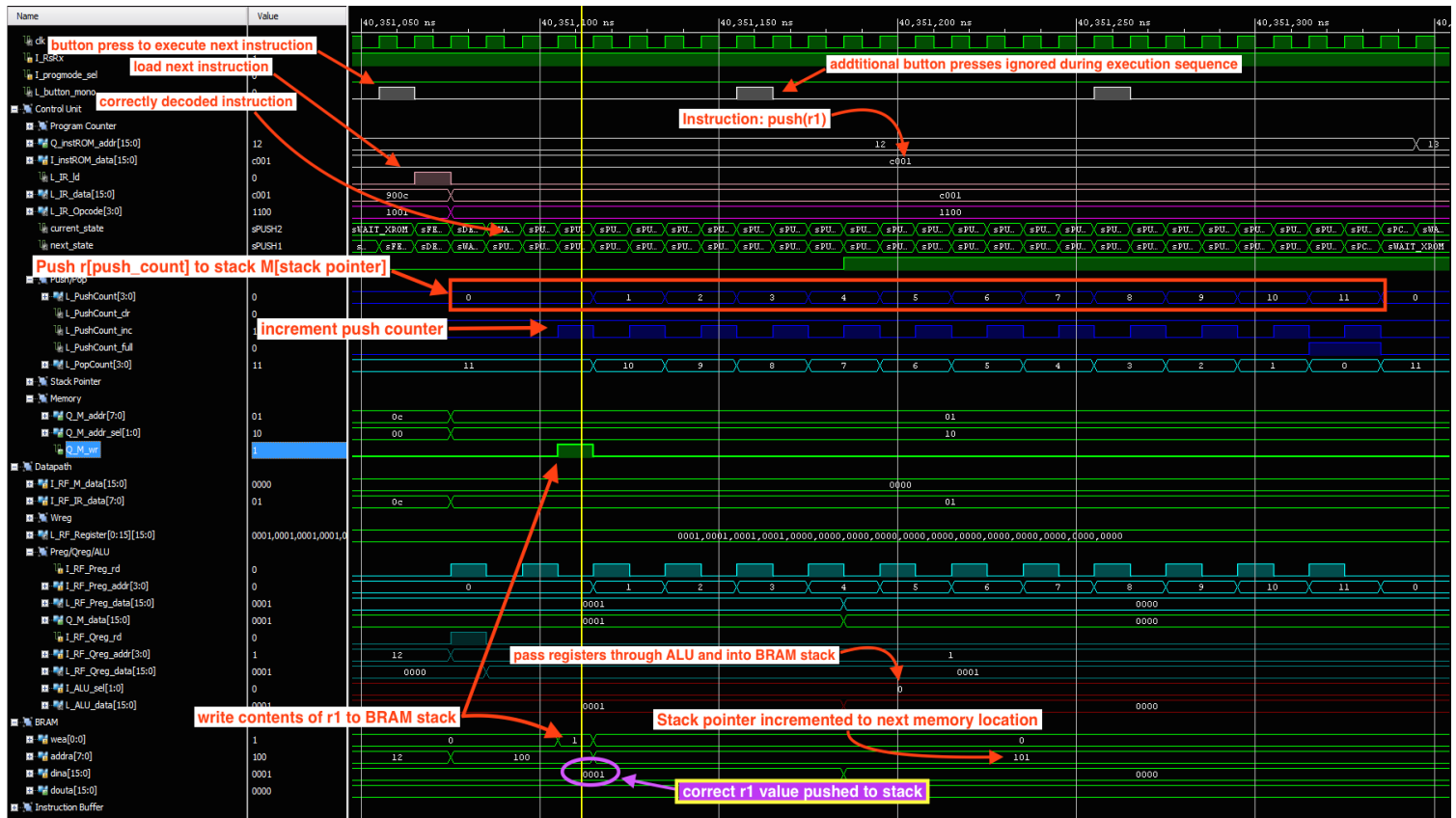

18: Pop

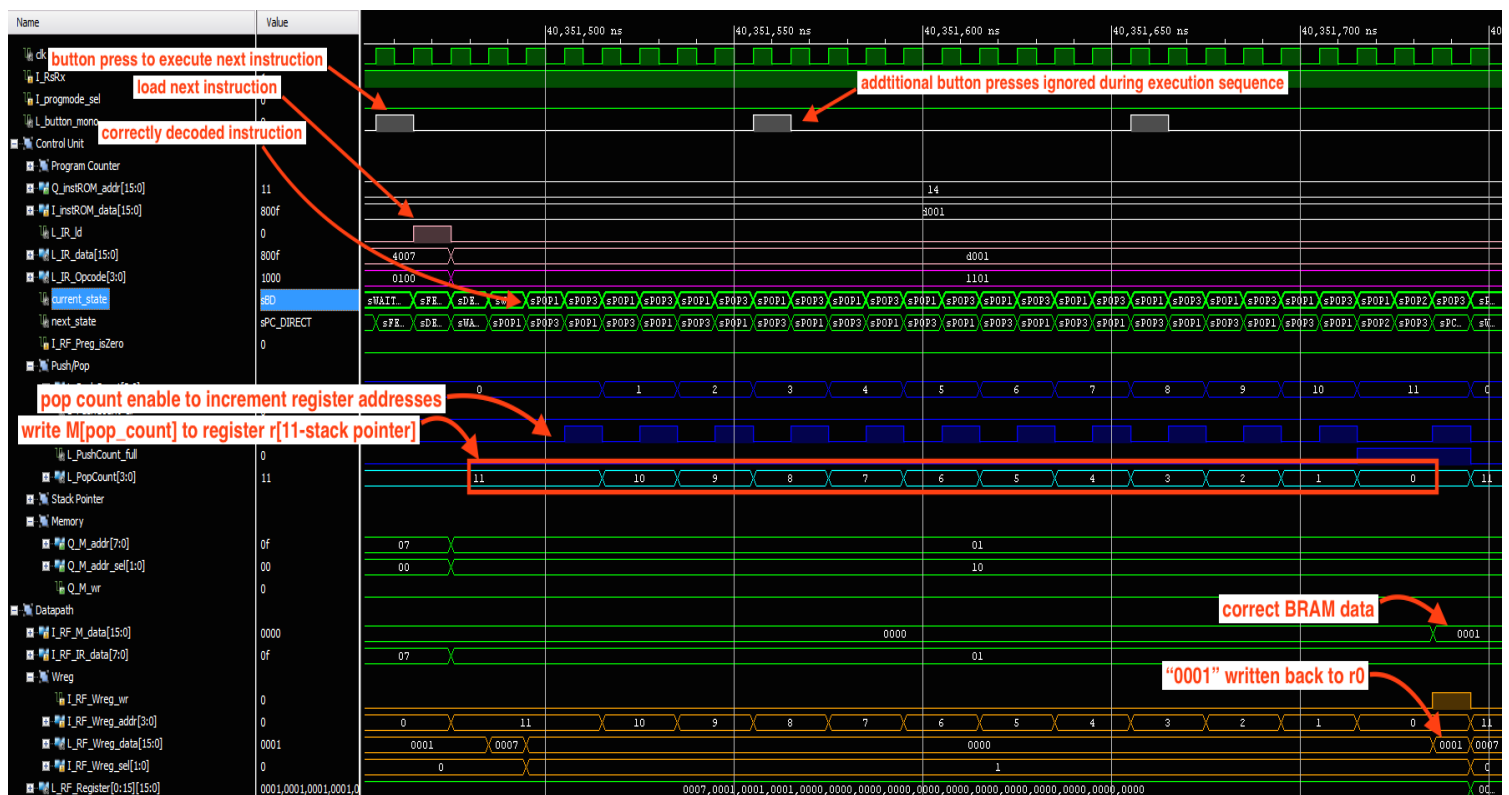


19: Restore PC after pop

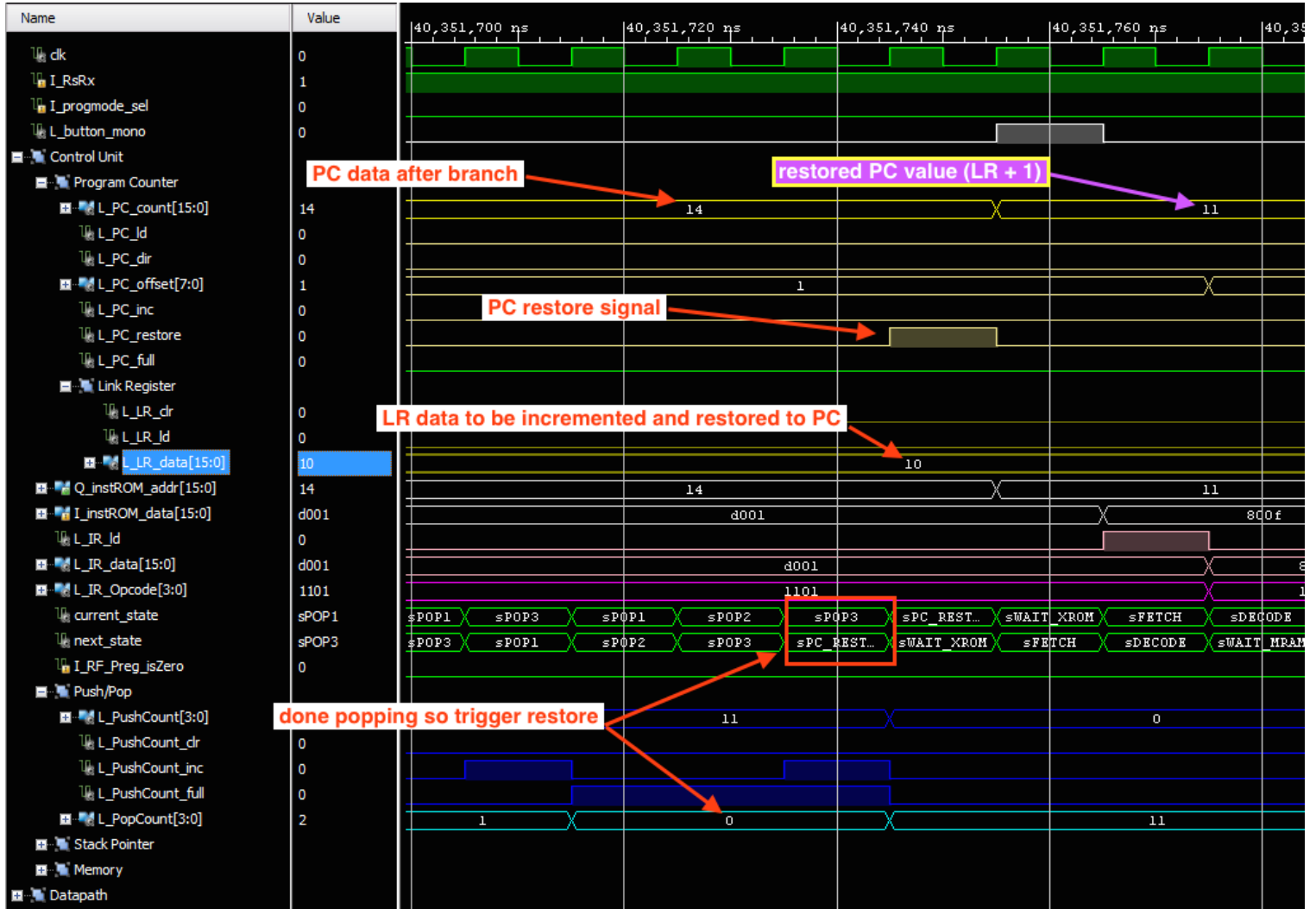


Hardware Implementation

Utilization Summary

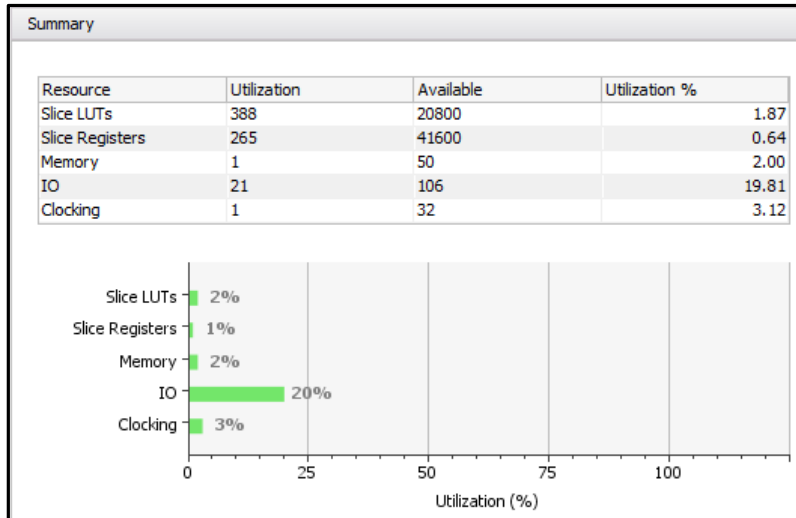

Hierarchy

Name	Slice LUTs (20800)	Slice Registers (41600)	F7 Muxes (16300)	F8 Muxes (8150)	Slice (8150)	LUT as Logic (20800)	LUT as Memory (9600)	LUT Flip Flop Pairs (20800)	Block RAM Tile (50)	Bonded IOB (106)	BUFGCTRL (32)
myRISC	388	265	14	1	139	352	36	444	1	21	1
SerialTx_T (SerialTx)	29	27	0	0	11	29	0	36	0	0	0
SerialRx_R (SerialRx)	22	37	0	0	12	22	0	33	0	0	0
Monopulser (Monopulse)	1	2	0	0	2	1	0	2	0	0	0
InstructionBuffer_B (Instru...)	75	71	0	0	33	75	0	89	0	0	0
Instruction_BRAM_X (instru...)	0	0	0	0	0	0	0	0	0.5	0	0
Error_Generator_E (errorgen)	11	5	0	0	5	11	0	11	0	0	0
Display (mux7seg)	8	21	0	0	9	8	0	26	0	0	0
Debouncer (debounce)	4	5	0	0	3	4	0	6	0	0	0
Datapath_D (Datapath)	55	32	0	0	17	19	36	55	0	0	0
ControlUnit_C (ControlUnit)	183	65	14	1	68	183	0	200	0	0	0
BRAM_M (BRAM)	0	0	0	0	0	0	0	0	0.5	0	0

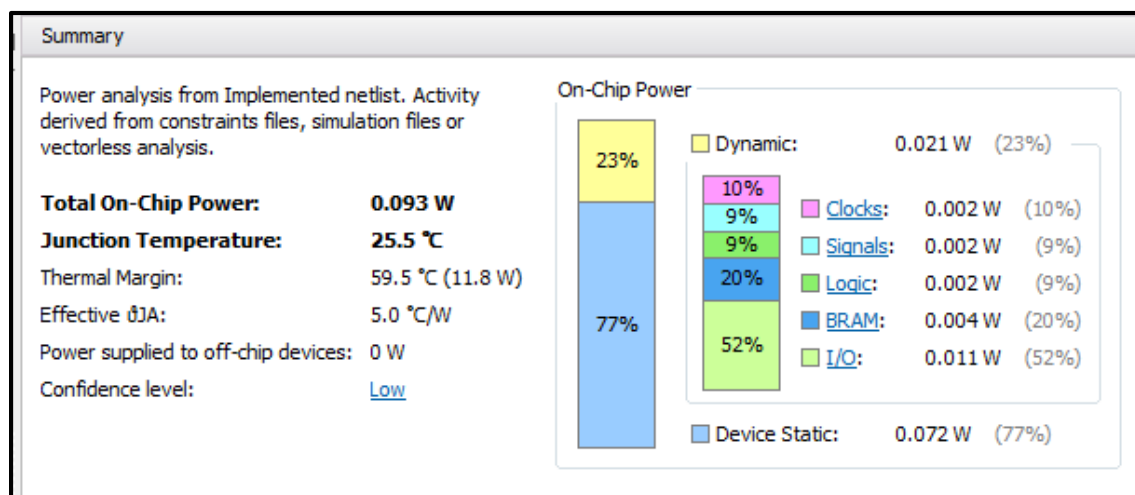

Timing Summary

Design Timing Summary			
Setup		Hold	Pulse Width
Worst Negative Slack (WNS): 3.275 ns		Worst Hold Slack (WHS): 0.079 ns	Worst Pulse Width Slack (WPWS): 3.750 ns
Total Negative Slack (TNS): 0.000 ns		Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0		Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 1060		Total Number of Endpoints: 1060	Total Number of Endpoints: 342
All user specified timing constraints are met.			

Critical Path (Setup)

Summary

NamePath 1

Slack3.275ns

SourceControlUnit_C/current_state_reg[3]/C (rising edge-triggered cell FDRE clocked by sys_clk_pin {rise@0.000ns fall@5.000ns period=10.000ns})

DestinationDatapath_D/L_RF_Register_reg_r3_0_15_12_15/RAMA_D1/I (rising edge-triggered cell RAMD32 clocked by sys_clk_pin {rise@0.000ns fall@5.000ns period=10.000ns})

Path Groupsys_clk_pin

Path TypeSetup (Max at Slow Process Corner)

Requirement10.000ns (sys_clk_pin rise@10.000ns - sys_clk_pin rise@0.000ns)

Data Path Delay6.464ns (logic 2.204ns (34.097%) route 4.260ns (65.903%))

Logic Levels7 (CARRY4=4 LUT5=1 LUT6=2)

Clock Path Skew0.032ns

Clock Uncertainty0.035ns

Source Clock Path

Data Path

Delay Type	Incr (ns)	Path (ns)	Location	Netlist Resource(s)
FDRE (Prop_fdre_C_O)	(f) 0.456	5.540	Site: SLICE_X57Y33	ControlUnit_C/current_state_reg[3]/Q
net (fo=65, routed)		1.613	7.153	ControlUnit_C/current_state[3]
LUT5 (Prop_lut5_I3_O)	(r) 0.124	7.277	Site: SLICE_X59Y40	ControlUnit_C/L_RF_Register_reg_r1_0_15_0_5_j_28/I3
net (fo=17, routed)		1.056	8.333	ControlUnit_C/L_RF_Register_reg_r1_0_15_0_5_j_28/O
CARRY4 (Prop_carry4_DI[0]_CO[3])	(r) 0.635	8.968	Site: SLICE_X59Y35	Datapath_D/p_0_in1_in
net (fo=1, routed)		0.000	8.968	Datapath_D/L_RF_Register_reg_r1_0_15_0_5_j_27/DI[0]
CARRY4 (Prop_carry4_CI_CO[3])	(r) 0.114	9.082	Site: SLICE_X59Y36	Datapath_D/L_RF_Register_reg_r1_0_15_0_5_j_27/CO[3]
net (fo=1, routed)		0.000	9.082	Datapath_D/n_0_L_RF_Register_reg_r1_0_15_0_5_j_27
CARRY4 (Prop_carry4_CI_CO[3])	(r) 0.114	9.196	Site: SLICE_X59Y37	Datapath_D/L_RF_Register_reg_r1_0_15_0_5_j_29/CI
net (fo=1, routed)		0.000	9.196	Datapath_D/L_RF_Register_reg_r1_0_15_0_5_j_29/CO[3]
CARRY4 (Prop_carry4_CI_O[1])	(r) 0.334	9.530	Site: SLICE_X59Y38	Datapath_D/n_0_L_RF_Register_reg_r1_0_15_0_5_j_29
net (fo=1, routed)		0.499	10.028	Datapath_D/L_RF_Register_reg_r1_0_15_6_11_j_13/CI
LUT6 (Prop_lut6_I2_O)	(r) 0.303	10.331	Site: SLICE_X58Y38	Datapath_D/n_0_L_RF_Register_reg_r1_0_15_6_11_j_13/CO[3]
net (fo=1, routed)		0.443	10.774	Datapath_D/L_RF_Register_reg_r1_0_15_6_11_j_13
LUT6 (Prop_lut6_I0_O)	(r) 0.124	10.898	Site: SLICE_X58Y40	Datapath_D/L_RF_Register_reg_r1_0_15_12_15_j_9/CI
net (fo=3, routed)		0.650	11.548	Datapath_D/L_RF_Register_reg_r1_0_15_12_15_j_9/O[1]
RAMD32			Site: SLICE_X64Y37	ControlUnit_C/p_0_in2_out[13]
Arrival Time		11.548		ControlUnit_C/L_RF_Register_reg_r1_0_15_12_15_j_12

Destination Clock Path

Delay Type	Incr (ns)	Path (ns)	Location	Netlist Resource(s)
(clock sys_clk_pin rise edge)	(r) 10.000	10.000		
net (fo=0)	(r) 0.000	10.000	Site: W5	clk
		0.000	10.000	clk_IBUF_inst/I
IBUF (Prop_ibuf_I_O)	(r) 1.388	11.388	Site: W5	clk_IBUF_inst/O
net (fo=1, routed)		1.862	13.250	clk_IBUF
BUFG (Prop_bufg_I_O)	(r) 0.091	13.341	Site: BUFGCTRL_X0Y0	clk_IBUF_BUGF_inst/I
net (fo=341, routed)		1.515	14.856	clk_IBUF_BUGF_inst/O
clock pessimism	0.260	15.116	Site: SLICE_X64Y37	Datapath_D/L_RF_Register_reg_r3_0_15_12_15/WCLK
clock uncertainty	-0.035	15.081		Datapath_D/L_RF_Register_reg_r3_0_15_12_15/RAMA_D1/CLK
RAMD32 (Setup_ramd32_CLK_1)	-0.258	14.823	Site: SLICE_X64Y37	Datapath_D/L_RF_Register_reg_r3_0_15_12_15/RAMA_D1
Required Time		14.823		

Component Architecture

Control Unit

Functionality

The control unit controls the flow of data through the datapath during the execution mode of the processor. This component contains the controller FSM along with the program counter, link register, instruction register, and stack pointer. Flow of data is controlled over a series of MUX select inputs which determine what information is able to enter the register file and ALU. The control unit also handles access requests from both the instruction RAM and general purpose RAM.

FSM

The finite state machine generates all of the control signals for the adjacent registers in the control unit and for the datapath and memory. The general operation of the FSM consists of these basic states – program count, fetch instruction, decode, and execute. The program count state controls the program counter, either incrementing it or loading in a predetermined memory address (depending on the previous instruction). After operating the program counter, the processor waits for the pushbutton before it fetches the next instruction from the memory. In the fetch instruction state the instruction register grabs the data from the address in the memory determined by the program counter. In the decode state the processor looks at the Opcode of the instruction held in the IR and moves to the appropriate execute state. In the execute state the FSM interacts with the datapath and the memory, moving the appropriate data between the two locations.


(See **Appendix L** for FSM diagram)

Datapath

Functionality

The datapath reacts to control signals from the control unit FSM and moves data between the 16 general purpose registers and the general purpose BRAM through two output pipeline registers (Preg and Qreg), an arithmetic logic unit (ALU), and an input multiplexer, all controlled by the control unit FSM. The synthesis tool chose to implement the general purpose registers as single-port write-enable/3-port read random access memory (RAM), though this could also be implemented as regular registers. The two read-output pipeline registers, Preg and Qreg, both send data into the ALU, which can add or subtract the data in the two registers or pass through the Preg data to be written back into a different register. The Preg is also used to send data directly into the BRAM, while the Qreg is used for indirect addressing of the BRAM. Data to be written to a register can come from the ALU, the BRAM, or directly from the instruction register in the control unit. These inputs are selected by a FSM-controlled multiplexer.

RTL Schematic

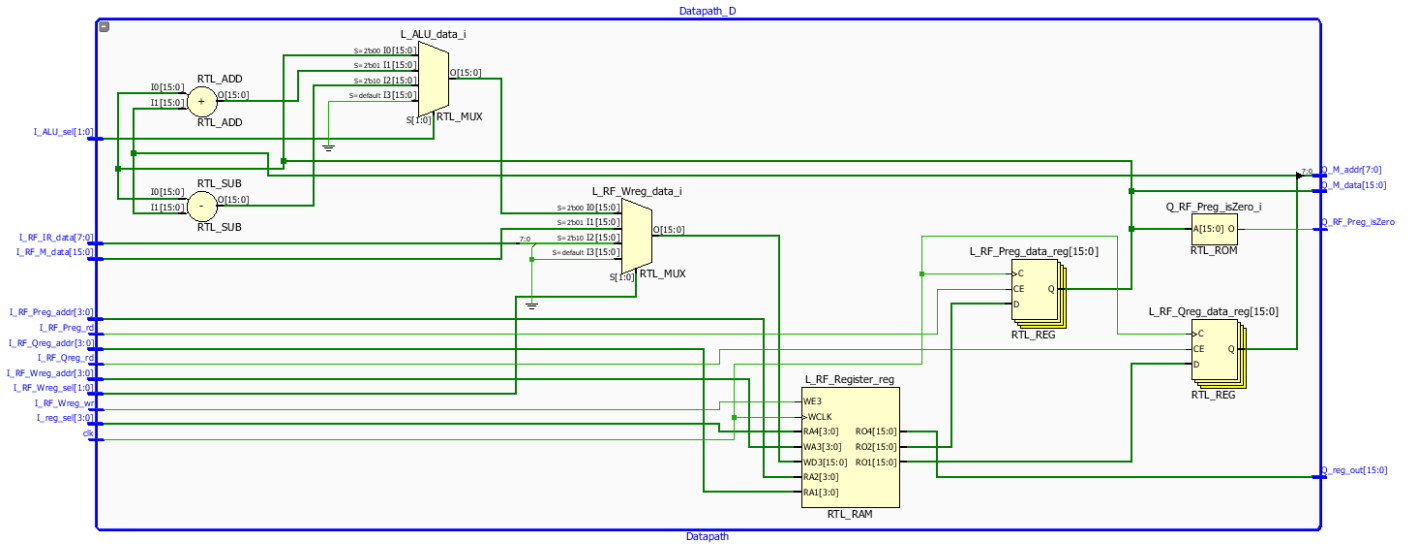


Instruction Buffer

Functionality

The instruction buffer receives 8-bit parallel data from the serial receiver and buffers it into a 4-word character buffer. Once four characters have been shifted in (detected by a counter that increments with every shift), the instruction buffer waits for a carriage return (CR) from the serial receiver. If the carriage return is recognized, the four previous characters are loaded out of the character buffer, converted from ASCII codes into the appropriate hexadecimal numbers, concatenated, and saved to the instruction memory (XRAM). A counter holds the address for the XRAM and increments every time an instruction is written. This counter holds its value once the user enters *execution* mode and is read by the control unit as a limit for the program counter. This value is cleared once the user re-enters *program* mode. If the received characters do not fit the (4-character then CR) format, the instruction is ignored and the instruction buffer asserts an error flag, which triggers a separate error sequence (see Error Generator).

FSM

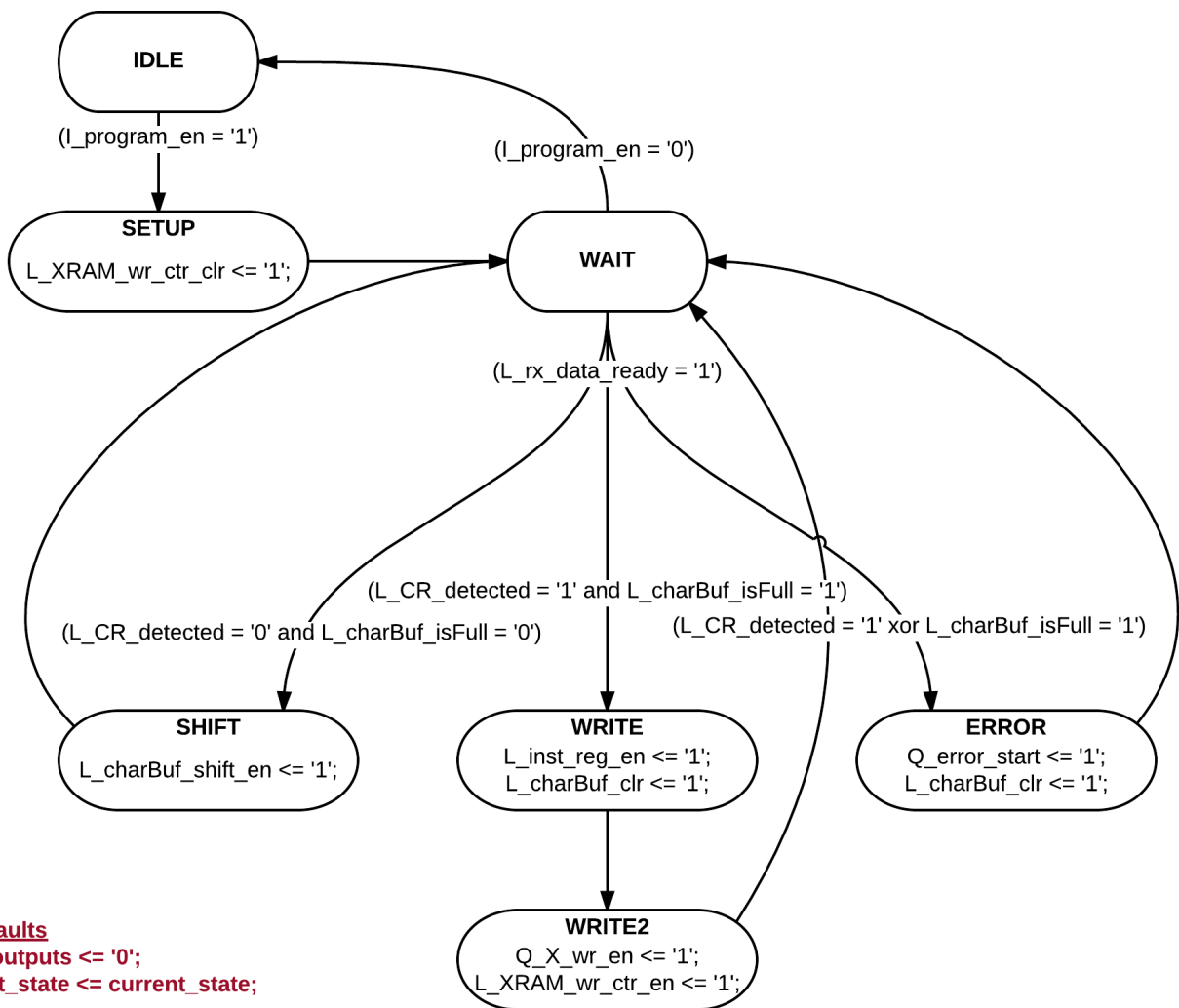Instruction Buffer FSM**General Purpose Memory (BRAM)****Functionality**

The single-port read/write enable block RAM serves for both general purpose memory and houses the Stack memory. The BRAM is controlled by the control unit and its data interacts purely with the datapath. The BRAM is written to with an enable signal from the control unit FSM. Its data input reads from the P register in the datapath. The BRAM address is MUX'ed between the instruction register (direct addressing), the Q register output (indirect addressing), and the Stack Pointer, selected asynchronously based the Opcode in the instruction register.

Instruction Memory (XRAM)

Functionality

The instruction memory is a single-port read/write enable block RAM that serves to hold the instructions sent in through the serial receiver and the instruction buffer. The address port is MUX'ed between the address output of the instruction buffer during *program* mode and the control unit during *execution* mode. The XRAM is written to using a write enable signal from the instruction buffer. The data out of the XRAM is sent to the control unit and into the instruction register.


Error Generation

Functionality

The error generator is a small module that sends an "ERROR\n" message through the serial transmitter when it is given a start tick signal. The module uses a counter to cycle through the 8-bit ASCII codes for each character in the "ERROR\n" string and sends each character to the serial transmitter one at a time.

FSM

Error Generator FSM

 

Defaults

all outputs $\leq '0'$

next_state \leq current_state

Results and Discussion

Ultimately, the project was successfully implemented in hardware. The processor functioned exactly as desired, and performed to the design specifications. In addition to rigorous testing of each instruction for a known set of inputs, the processor also was able to execute a program to compute the Fibonacci series (the series of numbers: 0, 1, 1, 2, 3, 5, 8, 13, 21, 34, ... where each number in the series is found by adding up the two numbers before it), which was the original “reach” design goal.

We are very happy with the level of success we have achieved in building a simple RISC processor. Success did not come without its share of hurdles, as there were many issues that we ran into along the way. One of the biggest struggles we faced was keeping track of the signal names and components, once the design reached a critical mass of complexity. This was resolved by adopting a very strict VHDL naming convention – detailed in Appendix A, which enabled us to easily determine the parent modules for signals and components. Another problem we ran into was debugging in hardware, given that most of the low-level operations that are critical to processor function can’t be observed from the top level design. This issue was overcome by methodically debugging each module individually, and by not proceeding with another portion of the design until we had verified hardware functionality for the current module. We also mapped a large number of control signals to the PMOD sockets so we could observe their values with an oscilloscope.

If we had more time to complete the project, we would have liked to incorporate a Multiple Intermediate Pipeline Stages (MIPS) architecture scheme into the design of the processor. This would require a parallel pipeline to be implemented both within the controller and the datapath. In a MIPS architecture, a new instruction is loaded into the IR on every clock cycle, and each stage of an instruction’s execution is simultaneously carried out and stored in the next pipeline register. This creates a faster processor by dramatically increasing instruction throughput, and also would allow us to clock our processor at higher speeds. Unfortunately, we determined that the control logic for a successful MIPS architecture stretches far beyond the scope of this course, and would have required an extra number of weeks to complete. The main difficulty in implementing a MIPS processor architecture arises when sequential instructions need to access the same register or memory address at a different stage in the pipeline. The controller now must not only ensure that both instructions are executed correctly, but also that the first instruction is fully executed before the second is performed – a daunting task when both instructions and data are moving through the pipeline at a different pace. Difficulties like this can be remedied by strategically placing No-Op commands in the pipeline to delay instructions that have these dependencies, ensuring the correct data is in the registers at the correct time. Part of this procedure is often done in software by the assembler, which is far beyond the scope of this course. We chose to first make sure that our control unit could properly operate the datapath, and ultimately decided that it would be more reasonable to add user interface functionality rather than attempt the parallel pipelined design.

We chose to interface with the processor over the familiar serial interface programming functionality and with a single-step pushbutton control. This idea, while not typical for a regular microprocessor, allowed us to demonstrate the functionality of the board in hardware rather than purely in simulation. While we initially attempted the very ambitious plan of creating a basic assembler in hardware, we quickly realized that this design would have been woefully inefficient and was not worth the effort.

While we are disappointed that we did not achieve the ambitious goal of creating our own assembler, we are glad that we were able to implement a fully functional design.

The biggest takeaways from this project have been a deepened understanding of processor operating principles, and exposure to different types of architectures. This project forced us to build for ourselves the defining features of a RISC microprocessor and required us to research many advanced features and architecture types before deciding on a specific design. Had we not chosen this ambitious project, we most likely would not have been exposed to any of the material and resources that we needed to utilize to achieve a successful result.

Appendix

Appendix A: VHDL Style Guidelines

Appendix B: VHDL Source Listings

Top Level

Controller

Datapath

Instruction Buffer

Error Generator

Serial Receiver

Serial Transmitter

Monopulser

Debouncer

7-segment display

Appendix C: Control Unit FSM Diagram

Appendix A: VHDL Style Conventions

Due to the large quantity of complex code, a strict VHDL naming convention was followed to prevent mixing up signals in different scopes.

Entities, components, signals, ports, and VHDL keywords are written in lowercase. Each has a prefix according to the following rules:

- **I_** for input ports of a VHDL **entity**
- **Q_** for output ports of a VHDL **entity**
- **L_** for local signals within an entity or generated by a VHDL construct (e.g. by a signal assignment)
 - counters, internal control signals,
- **X_** with an uppercase X for signals generated **by an instantiated entity**.
 - control signals, flags, TC, coming from a component

Each instantiated component is given some uppercase letter X (other than I, L, or Q) which will prefix all signals driven by that component. All signals driven by some component X can then either get the prefix **X_** (if the component drives an internal signal), or the prefix **Q_** (if the instantiated component drives an output port of the entity being defined). The resulting convention is that all signal names are prefixed by the component that drives them, unless it is connected to an output port of the current entity.

Enumerated types (states), constants, and variables are written in UPPERCASE. Prefixes have no underscores.

- states are prefixed by a lowercase "s" (sWAIT, sPOP)
- generic constants are prefixed by a lowercase "g" (gBUS_WIDTH)
- Numeric constants are prefixed by "r" if real, "I" if integer type, or "c" if STD_LOGIC
- variables are prefixed by lowercase "v" (vLOOP_NUM)

Appendix B: VHDL Source Listings

Top Level

```
-- Class:          ENGS 128 15S
-- Engineer:       Brett Nicholas and Matt Metzler
--
-- Create Date:    05/27/2015 03:43:05 PM
-- Design Name:    Final Project
-- Module Name:    myRISC - Behavioral
-- Project Name:   MyRISC
-- Target Devices: Xilinx Arctix7 FPGA on Digilent BASYS3 project board
-- Tool Versions:  Xilinx Vivado
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
library IEEE;
    use IEEE.STD_LOGIC_1164.ALL;
    use IEEE.NUMERIC_STD.ALL;

library UNISIM;
    use UNISIM.VComponents.all;

entity myRISC is
Port (
    clk           : in std_logic;           -- clock in
    I_RsRx        : in std_logic;           -- serial data in
    I_progmode_sel : in std_logic;           -- select between program and execute modes
    I_button       : in std_logic;           -- button to step through commands
    I_display_sel  : in std_logic;           -- select whether to display PC or registers
    I_reg_sel      : in std_logic_vector(3 downto 0); -- select which register to display
    Q_RsTx        : out std_logic;           -- serial data out
    Q_segments     : out std_logic_vector(0 to 6); -- segments for display
    Q_anodes       : out std_logic_vector(3 downto 0); -- anodes for display
);
end myRISC;

architecture Behavioral of myRISC is

-- Control Unit contains FSM controller for fetch,decode/load/execute/store operations
-- as well as the Program Counter (PC), Instruction Register (IR) and necessary switching logic
component ControlUnit is
Port (
    clk           : in std_logic;
    I_instrROM_data : in std_logic_vector (15 downto 0); -- instruction from ROM memory
    I_RF_Preg_isZero : in std_logic; -- flag indicating Preg is zero (used for jump if zero)
    I_program_en    : in std_logic; -- Enables programming mode (no program execution during this time)
    I_button        : in std_logic; -- button to step through commands
    I_PC_limit      : in std_logic_vector (7 downto 0); -- Maximum step to execute
    Q_instrROM_addr : out std_logic_vector (15 downto 0); -- ROM address from which to receive instructions
    Q_instrROM_rd   : out std_logic; -- ROM read enable signal to aquire instruction
    Q_M_addr        : out std_logic_vector (7 downto 0); -- BRAM address
    Q_M_addr_sel    : out std_logic_vector (1 downto 0); -- Select between direct and indirect memory access
    Q_M_wr          : out std_logic; -- BRAM write enable
    Q_RF_IR_data    : out std_logic_vector (7 downto 0); -- Bottom 8 bits from the instruction register (for load constant)
    Q_RF_Wreg_sel   : out std_logic_vector (1 downto 0); -- Mux select for inputs to register file
    Q_RF_Wreg_addr  : out std_logic_vector (3 downto 0); -- Address of register to be written to (Wreg)
    Q_RF_Wreg_wr    : out std_logic; -- write enable for write register (Wreg)
    Q_RF_Preg_addr  : out std_logic_vector (3 downto 0); -- Address of primary read register (Preg)
    Q_RF_Preg_rd    : out std_logic; -- read enable for Preg
    Q_RF_Qreg_addr  : out std_logic_vector (3 downto 0); -- Address of secondary read register (Qreg - only used for arithmetic functions)
    Q_RF_Qreg_rd    : out std_logic; -- read enable for Qreg
    Q_ALU_sel       : out std_logic_vector (1 downto 0); -- ALU MUX: 00=>Preg pass through, 01=>Preg+Qreg, 10=>Preg-Qreg
    Q_SP_addr       : out std_logic_vector (7 downto 0); -- Stack Pointer address for memory
    Q_PC_count      : out std_logic_vector (15 downto 0); -- Push the program count out to display
);
end component;

    signal C_instrROM_addr : std_logic_vector (15 downto 0); -- ROM address from which to receive instructions
    signal C_instrROM_rd   : std_logic; -- ROM read enable signal to aquire instruction
    signal C_M_addr        : std_logic_vector (7 downto 0); -- BRAM address
    signal C_M_addr_sel    : std_logic_vector (1 downto 0); -- Select between direct and indirect memory access
    signal C_M_wr          : std_logic; -- BRAM write enable
    signal C_RF_IR_data    : std_logic_vector (7 downto 0); -- Bottom 8 bits from the instruction register (for load constant)
    signal C_RF_Wreg_sel   : std_logic_vector (1 downto 0); -- Mux select for inputs to register file
    signal C_RF_Wreg_addr  : std_logic_vector (3 downto 0); -- Address of register to be written to (Wreg)
    signal C_RF_Wreg_wr    : std_logic; -- write enable for write register (Wreg)
    signal C_RF_Preg_addr  : std_logic_vector (3 downto 0); -- Address of primary read register (Preg)
    signal C_RF_Preg_rd    : std_logic; -- read enable for Preg
    signal C_RF_Qreg_addr  : std_logic_vector (3 downto 0); -- Address of secondary read register (Qreg - only used for arithmetic functions)
    signal C_RF_Qreg_rd    : std_logic; -- read enable for Qreg
    signal C_ALU_sel       : std_logic_vector (1 downto 0); -- ALU MUX: 00=>Preg pass through, 01=>Preg+Qreg, 10=>Preg-Qreg
    signal C_SP_addr       : std_logic_vector (7 downto 0); -- Stack Pointer address for memory
    signal C_PC_count      : std_logic_vector (15 downto 0); -- Push the program count out to display

-- Datapath contains data input MUX, MIPS, 16x1 Register File (RF), and ALU
component Datapath is
Port (
    clk           : in std_logic;
    I_RF_M_data   : in std_logic_vector (15 downto 0); -- data from BRAM into datapath
    I_RF_IR_data  : in std_logic_vector (7 downto 0); -- Bottom 8 bits from the instruction register (for load constant)
    I_RF_Wreg_addr : in std_logic_vector (3 downto 0); -- Address of register to be written to (Wreg)
    I_RF_Wreg_wr   : in std_logic; -- write enable for write register (Wreg)

```

```

    I_RF_Wreg_sel      : in std_logic_vector (1 downto 0);      -- Mux select for inputs to register file
    I_RF_Preg_addr     : in std_logic_vector (3 downto 0);      -- Address of primary read register (Preg)
    I_RF_Preg_rd       : in std_logic;                          -- read enable for Preg
    I_RF_Qreg_addr     : in std_logic_vector (3 downto 0);      -- Address of secondary read register (Qreg - only used for arithmetic functions)
    I_RF_Qreg_rd       : in std_logic;                          -- read enable for Qreg
    I_ALU_sel          : in std_logic_vector (1 downto 0);      -- ALU MUX: 00=>Preg pass through, 01=>Preg+Qreg, 10=>Preg-Qreg
    I_reg_sel          : in std_logic_vector (3 downto 0);      -- Select which register to display
    Q_M_data           : out std_logic_vector (15 downto 0);     -- data from datapath into BRAM
    Q_RF_Preg_isZero   : out std_logic;                          -- flag indicating Preg is zero (used for jump if zero)
    Q_M_addr           : out std_logic_vector (7 downto 0);     -- Memory address for indirect access
    Q_reg_out          : out std_logic_vector (15 downto 0);     -- register output for displaying
  );
end component;

signal D_RF_Preg_isZero : std_logic;                          -- flag indicating Preg is zero (used for jump if zero)
signal D_M_data         : std_logic_vector (15 downto 0);     -- data from datapath into BRAM
signal D_M_addr         : std_logic_vector (7 downto 0);     -- Memory address for indirect access
signal D_reg_out        : std_logic_vector (15 downto 0);     -- Register output for displaying

-- Instruction RAM for programmable processor instructions
-- Single-Port read/write BRAM, with read priority
COMPONENT instruction_BRAM
  PORT (
    clka      : IN std_logic;
    wea       : IN std_logic_vector(0 downto 0);
    addra     : IN std_logic_vector(7 downto 0);
    dina      : IN std_logic_vector(15 downto 0);
    douta     : OUT std_logic_vector(15 downto 0)
  );
end component;
signal X_instROM_data : std_logic_vector (15 downto 0);      -- instruction from ROM memory

-- Multipurpose single-port read/write BRAM, with read priority
-- Read/write operations have a 2 clock cycle latency
component BRAM
  port (
    clka      : in std_logic;          -- master clock
    ena       : in std_logic;          -- clock enable
    wea       : in std_logic_vector(0 downto 0); -- write enable
    addra     : in std_logic_vector(7 downto 0); -- read/write address
    dina      : in std_logic_vector(15 downto 0); -- write data in
    douta     : out std_logic_vector(15 downto 0) ); -- read data
end component;
signal M_RF_M_data : std_logic_vector (15 downto 0); -- data from BRAM into datapath

-- Serial Receiver to program XRAM over USART
component SerialRx
  port (
    clk      : in std_logic;
    RSrx     : in std_logic;
    Q_rx_data : out std_logic_vector(7 downto 0);
    Q_rx_done_tick : out std_logic );
end component;
signal R_RX_data : std_logic_vector (7 downto 0) := x"00";
signal R_RX_done_tick : std_logic := '0';

-- Serial Transmitter
component SerialTx is
  Port (
    clk      : in std_logic;
    tx_data  : in std_logic_vector (7 downto 0);
    tx_start : in std_logic;
    tx       : out std_logic; -- to Nexys 2 RS-232 port
    tx_done_tick : out std_logic);
end component;
signal T_tx_done_tick : std_logic := '0'; -- Transmitter done tick

-- Instruction buffer : Buffers received characters until carriage return, then converts
-- the received word into a 16-bit instruction and stores the word in instruction memory
component InstructionBuffer is
  Port (
    clk      : in std_logic;
    I_RX_done_tick : in std_logic;          -- SPI conversion done tick
    I_RX_data  : in std_logic_vector (7 downto 0); -- SPI parallel data
    I_program_en : in std_logic;          -- Enables programming mode (no program execution during this time)
    Q_instruction_word : out std_logic_vector (15 downto 0); -- 16-bit instruction to be stored in XRAM
    Q_X_addr   : out std_logic_vector (7 downto 0); -- XRAM write address
    Q_X_wr_en  : out std_logic;          -- XRAM write enable
    Q_X_busy   : out std_logic;          -- Instruction programming in progress flag
    Q_error_start : out std_logic;       -- start the error sequence
  );
end component;
signal B_instruction_word : std_logic_vector (15 downto 0) := x"0000"; -- 16-bit instruction to be stored in XRAM
signal B_X_addr          : std_logic_vector (7 downto 0) := x"00"; -- XRAM write address
signal B_X_wr_en         : std_logic := '0'; -- XRAM write enable
signal B_X_busy          : std_logic := '0'; -- Instruction programming in progress flag
signal B_error_start     : std_logic := '0';

component debounce IS
  PORT(
    clk      : IN std_logic; -- assumes 25Mhz clock (MIGHT NEED TO CHANGE)
    button   : IN std_logic; -- input signal to be debounced
    db_out   : OUT std_logic; -- debounced signal out
  );
end component;
signal L_button_db : std_logic := '0'; -- debounced button

```

```

component Monopulse IS
Port (
    clk          : in std_logic;
    button       : in std_logic;
    mono_out     : out std_logic
);
end component;
    signal L_button_mono : std_logic := '0'; -- monopolised and debounced button

component mux7seg is
Port (
    clk          : in std_logic;
    y0, y1, y2, y3 : in std_logic_vector (3 downto 0); -- digits
    seg         : out std_logic_vector(0 to 6); -- segments (a...g)
    an         : out std_logic_vector (3 downto 0) ); -- anodes
end component;
    signal L_display : std_logic_vector (15 downto 0) := x"0000";-- post-mux display vector

component errorgen is
Port (
    clk          : in std_logic;
    I_error_start : in std_logic;
    I_tx_done_tick : in std_logic;
    Q_tx_start    : out std_logic;
    Q_tx_data     : out std_logic_vector (7 downto 0)
);
end component;
    signal E_tx_start : std_logic := '0';
    signal E_tx_data  : std_logic_vector(7 downto 0) := x"00";

-- ADDRESS MUXes
    signal L_M_addr : std_logic_vector (7 downto 0) := x"00"; -- Memory address mux
    signal L_X_addr : std_logic_vector (7 downto 0) := x"00"; -- Instruction Memory address mux

BEGIN -----

-- Memory address MUX
-- switches between direct address, indirect address (within register), and the address held in the stack pointer.
with C_M_addr_sel select
    L_M_addr <=
        C_M_addr when "00",
        D_M_addr when "01",
        C_SP_addr when "10",
        x"00" when others;

-- Instruction Memory address MUX
-- Switches between address from controller (execute mode) and address from buffer (programmable mode)
with I_progmode_sel select
    L_X_addr <=
        C_instROM_addr(7 downto 0) when '0', -- address from controller (PC: execute mode)
        B_X_addr when '1', -- address from buffer (programming mode)
        x"00" when others;

-- Display Mux Process
DisplayMux: process(I_display_sel, I_progmode_sel, B_X_addr, D_reg_out, C_PC_count)
begin
    if (I_progmode_sel = '1') then
        L_display <= x"00" & B_X_addr;
    elsif (I_display_sel = '1') then
        L_display <= D_reg_out;
    else
        L_display <= C_PC_count;
    end if;
end process;

ControlUnit_C: ControlUnit
Port map( clk => clk,
    I_instROM_data => X_instROM_data, -- instruction from ROM memory
    I_RF_Preg_isZero => D_RF_Preg_isZero, -- flag indicating Preg is zero (used for jump if zero)
    I_RF_Program_en => I_progmode_sel, -- Enables programming mode (no program execution during this time)
    I_button => L_button_mono, -- button for stepping through instructions
    I_PC_limit => B_X_addr, -- Maximum step to execute
    Q_instROM_addr => C_instROM_addr, -- ROM address from which to receive instructions
    Q_instROM_rd => C_instROM_rd, -- ROM read enable signal to aquire instruction
    Q_M_addr => C_M_addr, -- BRAM address
    Q_M_addr_sel => C_M_addr_sel, -- Select between direct and indirect memory access
    Q_M_wr => C_M_wr, -- BRAM write enable
    Q_RF_IR_data => C_RF_IR_data, -- Bottom 8 bits from the instruction register (for load constant)
    Q_RF_Wreg_sel => C_RF_Wreg_sel, -- Mux select for inputs to register file
    Q_RF_Wreg_addr => C_RF_Wreg_addr, -- Address of register to be written to (Wreg)
    Q_RF_Wreg_wr => C_RF_Wreg_wr, -- write enable for write register (Wreg)
    Q_RF_Preg_addr => C_RF_Preg_addr, -- Address of primary read register (Preg)
    Q_RF_Preg_rd => C_RF_Preg_rd, -- read enable for Preg
    Q_RF_Qreg_addr => C_RF_Qreg_addr, -- Address of secondary read register (Qreg - only used for arithmetic functions)
    Q_RF_Qreg_rd => C_RF_Qreg_rd, -- read enable for Qreg
    Q_ALU_sel => C_ALU_sel, -- ALU MUX: 00=>Preg pass through, 01=>Preg+Qreg, 10=>Preg-Qreg
    Q_SP_addr => C_SP_addr, -- Stack Pointer address for memory
    Q_PC_count => C_PC_count -- Push the program count out to display
);

Datapath_D: Datapath
Port Map( clk => clk,
    I_RF_M_data => M_RF_M_data, -- data from BRAM into datapath
    I_RF_IR_data => C_RF_IR_data, -- Bottom 8 bits from the instruction register (for load constant)
    I_RF_Wreg_addr => C_RF_Wreg_addr, -- Address of register to be written to (Wreg)
    I_RF_Wreg_wr => C_RF_Wreg_wr, -- write enable for write register (Wreg)

```



```

I_RF_Wreg_sel => C_RF_Wreg_sel,      -- Mux select for inputs to register file
I_RF_Preg_addr => C_RF_Preg_addr,    -- Address of primary read register (Preg)
I_RF_Preg_rd => C_RF_Preg_rd,        -- read enable for Preg
I_RF_Qreg_addr => C_RF_Qreg_addr,    -- Address of secondary read register (Qreg - only used for arithmetic functions)
I_RF_Qreg_rd => C_RF_Qreg_rd,        -- read enable for Qreg
I_ALU_sel => C_ALU_sel,              -- ALU MUX: 00=>Preg pass through, 01=>Preg+Qreg, 10=>Preg-Qreg
I_reg_sel => I_reg_sel,              -- Select which register to display
Q_M_data => D_M_data,                -- data from datapath into BRAM
Q_RF_Preg_isZero => D_RF_Preg_isZero, -- flag indicating Preg is zero (used for jump if zero)
Q_M_addr => D_M_addr,                -- Memory address for indirect access
Q_reg_out => D_reg_out               -- register output for displaying
);

```

Instruction_BRAM_X: instruction_BRAM

```

Port Map (clk => clk,
  wea(0) => B_X_wr_en,
  addra => L_X_addr,
  dina => B_instruction_word,
  douta => X_instROM_data
);

```

BRAM_M: BRAM

```

Port Map (clk => clk,          -- Port A (write port) clock
  ena => '1',                  -- clock enable
  wea(0) => C_M_wr,            -- write enable (read if low, write if high)
  addra => L_M_addr,           -- read/write address
  dina => D_M_data,            -- write data: data from datapath into BRAM
  douta => M_RF_M_data         -- read data: from BRAM to Datapath
);

```

SerialRx_R: SerialRx

```

Port Map (clk => clk,
  RsRx => I_RsRx,
  Q_rx_data => R_RX_data,
  Q_rx_done_tick => R_RX_done_tick
);

```

SerialTx_T: SerialTx

```

Port Map (clk => clk,
  tx_data => E_tx_data,
  tx_start => E_tx_start,
  tx => Q_RsTx, -- to Nexys 2 RS-232 port
  tx_done_tick => T_tx_done_tick
);

```

Error_Generator_E: errorgen

```

Port Map (clk => clk,
  I_error_start => B_error_start,
  I_tx_done_tick => T_tx_done_tick,
  Q_tx_start => E_tx_start,
  Q_tx_data => E_tx_data
);

```

InstructionBuffer_B: InstructionBuffer

```

Port Map (clk => clk,
  I_RX_done_tick => R_RX_done_tick, -- SPI conversion done tick
  I_RX_data => R_rx_data,           -- SPI parallel data
  I_program_en => I_progmode_sel,   -- Enables programming mode (no program execution during this time)
  Q_instruction_word => B_instruction_word, -- 16-bit instruction to be stored in XRAM
  Q_X_addr => B_X_addr,              -- XRAM write address (also PC limit)
  Q_X_wr_en => B_X_wr_en,            -- XRAM write enable
  Q_X_busy => B_X_busy,              -- Instruction programming in progress flag
  Q_error_start => B_error_start     -- start the error sequence
);

```

Debouncer: debounce

```

Port Map (clk => clk,
  button => I_button,
  db_out => L_button_db
);

```

Monopulser: monopulse

```

Port Map (clk => clk,
  button => L_button_db,
  mono_out => L_button_mono
);

```

Display: mux7seg

```

Port Map (clk => clk,
  y0 => L_display(3 downto 0),
  y1 => L_display(7 downto 4),
  y2 => L_display(11 downto 8),
  y3 => L_display(15 downto 12),
  seg => Q_segments,
  an => Q_anodes
);

```

end Behavioral;

Controller

```
-- Class:          ENGS 128 15S
-- Engineer:       Brett Nicholas and Matt Metzler
--
-- Create Date:    05/27/2015 03:43:05 PM
-- Design Name:    Final Project
-- Module Name:    ControlUnit - Behavioral
-- Project Name:   MyRISC
-- Target Devices: Xilinx Arctix7 FPGA on Digilent BASYS3 project board
-- Tool Versions:  Xilinx Vivado
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
```

```
-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;
```

```
entity ControlUnit is
```

```
Generic (STACK_TOP : integer := 100); -- Address of the beginning of the stack
```

```
Port (
    clk           : in std_logic;
    I_instROM_data : in std_logic_vector (15 downto 0); -- instruction from ROM memory
    I_RF_Preg_isZero : in std_logic; -- flag indicating Preg is zero (used for jump if zero)
    I_program_en   : in std_logic; -- Enables programming mode (no program execution during this time)
    I_button       : in std_logic; -- button to step through commands
    I_PC_limit     : in std_logic_vector (7 downto 0); -- Maximum step to execute
    Q_instROM_addr : out std_logic_vector (15 downto 0); -- ROM address from which to receive instructions
    Q_instROM_rnd  : out std_logic; -- ROM read enable signal to aquire instruction
    Q_M_addr       : out std_logic_vector (7 downto 0); -- BRAM address
    Q_M_addr_sel   : out std_logic_vector (1 downto 0); -- Select between direct and indirect memory access
    Q_M_wr         : out std_logic; -- BRAM write enable
    Q_RF_IR_data   : out std_logic_vector (7 downto 0); -- Bottom 8 bits from the instruction register (for load constant)
    Q_RF_Wreg_sel  : out std_logic_vector (1 downto 0); -- Mux select for inputs to register file
    Q_RF_Wreg_addr : out std_logic_vector (3 downto 0); -- Address of register to be written to (Wreg)
    Q_RF_Wreg_wr   : out std_logic; -- write enable for write register (Wreg)
    Q_RF_Preg_addr : out std_logic_vector (3 downto 0); -- Address of primary read register (Preg)
    Q_RF_Preg_rd   : out std_logic; -- read enable for Preg
    Q_RF_Qreg_addr : out std_logic_vector (3 downto 0); -- Address of secondary read register (Qreg - only used for arithmetic functions)
    Q_RF_Qreg_rd   : out std_logic; -- read enable for Qreg
    Q_ALU_sel      : out std_logic_vector (1 downto 0); -- ALU MUX: 00=>Preg pass through, 01=>Preg+Qreg, 10=>Preg-Qreg
    Q_SP_addr      : out std_logic_vector (7 downto 0); -- Stack Pointer address for memory
    Q_PC_count     : out std_logic_vector (15 downto 0); -- Push the program count out to display
);
```

```
end ControlUnit;
```

```
architecture Behavioral of ControlUnit is
```

```
-- Signals for the Program Counter
signal L_PC_count : unsigned (15 downto 0) := x"0000"; -- Program Count
signal L_PC_ld    : std_logic := '0'; -- PC load from IR offset
signal L_PC_clr   : std_logic := '0'; -- clear the PC
signal L_PC_inc   : std_logic := '0'; -- increment the PC
signal L_PC_dir   : std_logic := '0'; -- PC jump to direct address
signal L_PC_restore : std_logic := '0'; -- PC restore from LR
signal L_PC_offset : unsigned (7 downto 0) := x"00"; -- PC offset value from IR
signal L_PC_full  : std_logic := '0'; -- Flag when PC reaches the limit

-- Signals for Instruction Register
signal L_IR_data : std_logic_vector (15 downto 0) := x"0000"; -- Instruction held in the IR
signal L_IR_ld   : std_logic := '0'; -- load enable for IR
signal L_IR_Opcode : std_logic_vector (3 downto 0);

-- Signals for the Link Register
signal L_LR_data : unsigned (15 downto 0) := x"0000"; -- Link Register
signal L_LR_ld   : std_logic := '0'; -- LR load from PC
signal L_LR_clr  : std_logic := '0'; -- clear the LR

-- Signals for the stack register
signal L_SP_addr : unsigned (7 downto 0) := to_unsigned(STACK_TOP, 8); -- Stack pointer
signal L_SP_inc  : std_logic := '0'; -- Stack pointer increment
signal L_SP_dec  : std_logic := '0'; -- Stack pointer decrement
signal L_SP_clr  : std_logic := '0'; -- Stack pointer clear

-- Signals for Push Counter
signal L_PushCount : unsigned (3 downto 0) := "0000"; -- Counter for Push/Pop operations (cycles through registers)
signal L_PushCount_clr : std_logic := '0'; -- Clear the Push Counter
signal L_PushCount_inc : std_logic := '0'; -- increment the Push Counter
signal L_PushCount_full : std_logic := '0'; -- Flag when Push Counter = 12
signal L_PopCount : unsigned (3 downto 0) := x"C"; -- Pop Count
signal L_Push_ready : std_logic := '0'; -- enable pushing!
signal L_Pop_ready  : std_logic := '0'; -- enable popping!
```

```

-- State Machine signals
type state_type is (sIDLE, sWAIT_XROM, sWAIT_MRAM, sPC_INC, sPC_INC_pre, sPC_DIRECT, sPC_DIRECT_pre, sPC_JUMP, sPC_JUMP_pre,
sPC_RESTORE, sPC_RESTORE_pre, sFETCH, sDECODE, sLOAD_DIR, sSTORE_DIR, sMOVE, sCONST, sADD, sSUB, sBZ,
sBD, sBL, sLOAD_IND, sSTORE_IND, sNO_OP, sPUSH1, sPUSH2, sPOP1, sPOP2, sPOP3, sFINISHED, sFIRST);

signal current_state, next_state : state_type := sIDLE;

begin

Q_instROM_rd <= '1';
L_IR_Opcode <= L_IR_data(15 downto 12);

-- Asynchronous Address Outputs
Q_instROM_addr <= std_logic_vector(L_PC_count);
Q_M_addr <= L_IR_data(7 downto 0);
Q_RF_Qreg_addr <= L_IR_data(3 downto 0);
Q_SP_addr <= std_logic_vector(L_SP_addr);
Q_RF_Wreg_addr <= std_logic_vector(L_PopCount) when (L_IR_Opcode = x"D") else L_IR_data(11 downto 8);

with L_IR_opcode select
    Q_RF_Preg_addr <=
        L_IR_data(11 downto 8) when x"2",
        L_IR_data(11 downto 8) when x"7",
        std_logic_vector(L_PushCount) when x"C",
        L_IR_data(7 downto 4) when others;

with L_IR_opcode select
    Q_M_addr_sel <=
        "01" when x"a",           -- Memory address gets Qreg
        "01" when x"b",
        "10" when x"c",           -- Memory address gets stack pointer
        "10" when x"d",
        "00" when others;

-----
ProgramCounter: process(clk)
begin
    if rising_edge(clk) then
        if ( L_PC_clr = '1' ) then
            L_PC_count <= x"0000";
        elsif ( L_PC_inc = '1' ) then
            L_PC_count <= L_PC_count + 1;
        elsif ( L_PC_dir = '1' ) then
            L_PC_count <= x"00" & L_PC_offset;
        elsif ( L_PC_ld = '1' ) then
            L_PC_count <= L_PC_count + 1 + L_PC_offset;
        elsif ( L_PC_restore = '1' ) then
            L_PC_count <= L_IR_data + 1;
        end if;
    end if;
end process;
Q_PC_count <= std_logic_vector(L_PC_count);
L_PC_full <= '1' when L_PC_count >= (unsigned(I_PC_limit) - 1) else '0';

LinkRegister: process(clk)
begin
    if rising_edge(clk) then
        if ( L_LR_clr = '1' ) then
            L_LR_data <= x"0000";
        elsif ( L_LR_ld = '1' ) then
            L_LR_data <= L_PC_count;
        end if;
    end if;
end process;

StackPointer: process(clk)
begin
    if rising_edge(clk) then
        if (L_SP_clr = '1') then
            L_SP_addr <= to_unsigned(STACK_TOP, L_SP_addr'Length); -- reset SP to STACK_TOP
        elsif (L_SP_dec = '1') then
            L_SP_addr <= L_SP_addr - 1; -- decrement SP
        elsif (L_SP_inc = '1') then
            L_SP_addr <= L_SP_addr + 1; -- increment SP
        end if;
    end if;
end process;

PushCounter: process(clk)
begin
    if rising_edge(clk) then
        if ( L_PushCount_clr = '1' ) then
            L_PushCount <= "0000";
        elsif ( L_PushCount_inc = '1' ) then
            if ( L_PushCount_full = '1' ) then
                L_PushCount <= "0000";
            else
                L_PushCount <= L_PushCount + 1;
            end if;
        end if;
    end if;
end process;

```

```

L_PushCount_full <= '1' when ( L_PushCount = x"B" ) else '0';           -- Push Count is full when 12
L_PopCount <= 11 - L_PushCount;
L_Push_ready <= '1' when ( L_IR_data(to_integer(L_PushCount)) = '1' ) else '0';
L_Pop_ready <= '1' when ( L_IR_data(to_integer(L_PopCount)) = '1' ) else '0';

```

```

InstructionRegister: process(clk)
begin
    if rising_edge(clk) then
        if ( L_IR_ld = '1' ) then
            L_IR_data <= I_instROM_data;
        end if;
    end if;
end process;
L_PC_offset <= unsigned(L_IR_data(7 downto 0));
Q_RF_IR_data <= L_IR_data(7 downto 0);

```

```

StateUpdate: process(clk)
begin
    if rising_edge(clk) then
        current_state <= next_state;
    end if;
end process;

```

```

StateMachine: process(current_state, L_IR_Opcode, I_RF_Preg_isZero, I_program_en, L_PushCount_full, L_Push_ready, L_Pop_ready, I_button, L_PC_full)
begin
    -- State Default
    next_state <= current_state;

    --Local signal defaults
    L_IR_ld <= '0';
    L_PC_clr <= '0';
    L_PC_inc <= '0';
    L_PC_ld <= '0';
    L_PC_dir <= '0';
    L_PC_restore <= '0';
    L_LR_ld <= '0';
    L_LR_clr <= '0';
    L_SP_clr <= '0';
    L_SP_inc <= '0';
    L_SP_dec <= '0';
    L_PushCount_clr <= '0';
    L_PushCount_inc <= '0';

    --Output defaults
    Q_RF_Preg_rd <= '0';
    Q_RF_Qreg_rd <= '0';
    Q_RF_Wreg_sel <= "00";
    Q_RF_Wreg_wr <= '0';
    Q_M_wr <= '0';
    Q_ALU_sel <= "00";

    case current_state is

        when SIDLE =>
            L_PC_clr <= '1';
            L_LR_clr <= '1';
            L_SP_clr <= '1';
            if ( I_program_en = '0' ) then
                next_state <= sWAIT_XROM;
            end if;

        when sWAIT_XROM =>
            if I_button = '1' then
                next_state <= sFETCH;
            end if;

        when sFETCH =>
            L_IR_ld <= '1';
            next_state <= sDECODE;

        when sDECODE =>
            Q_RF_Preg_rd <= '1';
            Q_RF_Qreg_rd <= '1';
            next_state <= sWAIT_MRAM;

        when sWAIT_MRAM =>

            case L_IR_Opcode is
                when x"0" => next_state <= sNO_OP;
                when x"1" => next_state <= sLOAD_DIR;
                when x"2" => next_state <= sSTORE_DIR;
                when x"3" => next_state <= sMOVE;
                when x"4" => next_state <= sCONST;
                when x"5" => next_state <= sADD;
                when x"6" => next_state <= sSUB;
                when x"7" => next_state <= sBZ;
                when x"8" => next_state <= sBD;
                when x"9" => next_state <= sBL;
                when x"A" => next_state <= sLOAD_IND;
                when x"B" => next_state <= sSTORE_IND;
                when x"C" => next_state <= sPUSH1;
                when x"D" => next_state <= sPOP1;
                when others => next_state <= sPC_INC;
            end case;

```

```

when sLOAD_DIR =>
    Q_RF_Wreg_wr <= '1';
    Q_RF_Wreg_sel <= "01";
    if L_PC_full = '1' then
        next_state <= sFINISHED;
    else next_state <= sPC_INC;
    end if;

when sSTORE_DIR =>
    Q_M_wr <= '1';
    if L_PC_full = '1' then
        next_state <= sFINISHED;
    else next_state <= sPC_INC;
    end if;

when sMOVE =>
    Q_RF_Wreg_wr <= '1';
    if L_PC_full = '1' then
        next_state <= sFINISHED;
    else next_state <= sPC_INC;
    end if;

when sCONST =>
    Q_RF_Wreg_sel <= "10";
    Q_RF_Wreg_wr <= '1';
    if L_PC_full = '1' then
        next_state <= sFINISHED;
    else next_state <= sPC_INC;
    end if;

when sADD =>
    Q_ALU_sel <= "01";
    Q_RF_Wreg_wr <= '1';
    if L_PC_full = '1' then
        next_state <= sFINISHED;
    else next_state <= sPC_INC;
    end if;

when sSUB =>
    Q_ALU_sel <= "10";
    Q_RF_Wreg_wr <= '1';
    if L_PC_full = '1' then
        next_state <= sFINISHED;
    else next_state <= sPC_INC;
    end if;

when sBZ =>
    if ( I_RF_Preg_isZero = '1' ) then
        next_state <= sPC_JUMP;
    else
        if L_PC_full = '1' then
            next_state <= sFINISHED;
        else next_state <= sPC_INC;
        end if;
    end if;

when sBD =>
    next_state <= sPC_DIRECT;

when sBL =>
    L_LR_ld <= '1';
    next_state <= sPC_DIRECT;

when sLOAD_IND =>
    Q_RF_Wreg_wr <= '1';
    Q_RF_Wreg_sel <= "01";
    if L_PC_full = '1' then
        next_state <= sFINISHED;
    else next_state <= sPC_INC;
    end if;

when sSTORE_IND =>
    Q_M_wr <= '1';
    if L_PC_full = '1' then
        next_state <= sFINISHED;
    else next_state <= sPC_INC;
    end if;

when sNO_OP =>
    if L_PC_full = '1' then
        next_state <= sFINISHED;
    else next_state <= sPC_INC;
    end if;

when sPC_INC =>
    L_PC_inc <= '1';
    next_state <= sWAIT_XROM;

when sPC_JUMP =>
    L_PC_ld <= '1';
    next_state <= sWAIT_XROM;

when sPC_DIRECT =>
    L_PC_dir <= '1';
    next_state <= sWAIT_XROM;

when sPC_RESTORE =>

```

```

        L_PC_restore <= '1';
        next_state <= sWAIT_XROM;

    when sPUSH1 =>
        Q_RF_Preg_rd <= '1';
        next_state <= sPUSH2;

    when sPUSH2 =>
        L_PushCount_inc <= '1';
        if ( L_Push_ready = '1' ) then
            Q_M_wr <= '1';
            L_SP_inc <= '1';
        end if;

        if ( L_PushCount_full = '1' ) then
            next_state <= sPC_INC;
        else
            next_state <= sPUSH1;
        end if;

    when sPOP1 =>
        Q_RF_Wreg_sel <= "01";
        if ( L_Pop_ready = '1' ) then
            L_SP_dec <= '1';
            next_state <= sPOP2;
        else
            next_state <= sPOP3;
        end if;

    when sPOP2 =>
        Q_RF_Wreg_sel <= "01";
        next_state <= sPOP3;

    when sPOP3 =>
        Q_RF_Wreg_sel <= "01";
        L_PushCount_inc <= '1';
        if ( L_Pop_ready = '1' ) then
            Q_RF_Wreg_wr <= '1';
        end if;

        if (L_PushCount_full = '1') then
            next_state <= sPC_RESTORE;
        else
            next_state <= sPOP1;
        end if;

    when sFINISHED =>

    when others =>
        next_state <= sPC_INC_pre;
    end case;

    if ( I_program_en = '1' ) then
        next_state <= sIDLE;
    end if;

end process;

end Behavioral;

```

Datapath

```
-- Class:          ENGS 128 15S
-- Engineer:       Brett Nicholas and Matt Metzler
--
-- Create Date:    05/27/2015 03:43:05 PM
-- Design Name:    Final Project
-- Module Name:    Datapath - Behavioral
-- Project Name:    MyRISC
-- Target Devices: Xilinx Arctix7 FPGA on Digilent BASYS3 project board
-- Tool Versions:  Xilinx Vivado
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Datapath is
  Port (
    clk           : in std_logic;
    I_RF_M_data   : in std_logic_vector (15 downto 0);
    I_RF_IR_data  : in std_logic_vector (7 downto 0);
    I_RF_Wreg_addr : in std_logic_vector (3 downto 0);
    I_RF_Wreg_wr   : in std_logic;
    I_RF_Wreg_sel  : in std_logic_vector (1 downto 0);
    I_RF_Preg_addr : in std_logic_vector (3 downto 0);
    I_RF_Preg_rd   : in std_logic;
    I_RF_Qreg_addr : in std_logic_vector (3 downto 0);
    I_RF_Qreg_rd   : in std_logic;
    I_ALU_sel      : in std_logic_vector (1 downto 0);
    I_reg_sel      : in std_logic_vector (3 downto 0);
    Q_M_data       : out std_logic_vector (15 downto 0);
    Q_RF_Preg_isZero : out std_logic;
    Q_M_addr       : out std_logic_vector (7 downto 0);
    Q_reg_out      : out std_logic_vector (15 downto 0);
  );
end Datapath;

architecture Behavioral of Datapath is

  -- Structure for register file
  type Register_File is array(0 to 15) of std_logic_vector(15 downto 0);
  signal L_RF_Register : Register_File := (others => (others => '0'));

  signal L_RF_Preg_data : unsigned(15 downto 0) := x"0000";
  signal L_RF_Qreg_data : unsigned(15 downto 0) := x"0000";
  signal L_ALU_data     : unsigned(15 downto 0) := x"0000";
  signal L_RF_Wreg_data : std_logic_vector(15 downto 0) := x"0000";

begin

  --Select register to display
  Q_reg_out <= L_RF_Register(to_integer(unsigned(I_reg_sel)));

  WregDataMux: process(I_RF_IR_data, I_RF_M_data, L_ALU_data, I_RF_Wreg_sel)
  begin
    case I_RF_Wreg_sel is
      when "00" =>
        L_RF_Wreg_data <= std_logic_vector(L_ALU_data);
      when "01" =>
        L_RF_Wreg_data <= I_RF_M_data;
      when "10" =>
        L_RF_Wreg_data <= x"00" & I_RF_IR_data;
      when others =>
        L_RF_Wreg_data <= x"0000";
    end case;
  end process;

  RegisterWrite: process(clk)
  begin
    if rising_edge(clk) then
      if ( I_RF_Wreg_wr = '1' ) then
        L_RF_Register(to_integer(unsigned(I_RF_Wreg_addr))) <= L_RF_Wreg_data;
      end if;
    end if;
  end process;

  PregQreg: process(clk)
  begin
```

```

    if rising_edge(clk) then
        -- Register Preg from the array
        if ( I_RF_Preg_rd = '1' ) then
            L_RF_Preg_data <= unsigned(L_RF_Register(to_integer(unsigned(I_RF_Preg_addr))));
        end if;
        -- Register Qreg from the array
        if ( I_RF_Qreg_rd = '1' ) then
            L_RF_Qreg_data <= unsigned(L_RF_Register(to_integer(unsigned(I_RF_Qreg_addr))));
        end if;
    end if;
end process;

ArithmeticLogicUnit: process(L_RF_Preg_data, L_RF_Qreg_data, I_ALU_sel)
begin
    case I_ALU_sel is
        when "00" =>
            L_ALU_data <= L_RF_Preg_data;
            -- Preg pass through
        when "01" =>
            L_ALU_data <= L_RF_Preg_data + L_RF_Qreg_data;
            -- Preg + Qreg
        when "10" =>
            L_ALU_data <= L_RF_Preg_data - L_RF_Qreg_data;
            -- Preg - Qreg
        when others =>
            L_ALU_data <= x"0000";
    end case;
end process;

-- Asynchronous Preg Zero flag
Q_RF_Preg_isZero <= '1' when L_RF_Preg_data = x"0000" else '0';

-- Data written to memory always comes from Preg
Q_M_data <= std_logic_vector(L_RF_Preg_data);
Q_M_addr <= std_logic_vector(L_RF_Qreg_data(7 downto 0));

end Behavioral;

```


Instruction Buffer

```
-- Class:          ENGS 128 15S
-- Engineer:       Brett Nicholas and Matt Metzler
-- S
-- Create Date:    05/27/2015 03:43:05 PM
-- Design Name:    Final Project
-- Module Name:    InstructionBuffer - Behavioral
-- Project Name:    MyRISC
-- Target Devices:  Xilinx Arctix7 FPGA on Digilent BASYS3 project board
-- Tool Versions:  Xilinx Vivado
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
library UNISIM;
use UNISIM.VComponents.all;

entity InstructionBuffer is
Port (
    clk                : in std_logic;
    I_RX_done_tick     : in std_logic;
    I_RX_data          : in std_logic_vector (7 downto 0);
    I_program_en       : in std_logic;
    Q_instruction_word  : out std_logic_vector (15 downto 0);
    Q_X_addr           : out std_logic_vector (7 downto 0);
    Q_X_wr_en          : out std_logic;
    Q_error_start      : out std_logic;
);
end InstructionBuffer;

architecture Behavioral of InstructionBuffer is

-- converts 8-bit ascii code for 0->f to hex representation
function ascii2hex (a: std_logic_vector(7 downto 0)) return std_logic_vector is
    variable tmp: std_logic_vector(3 downto 0) := x"0";
begin
    case a is
        when x"30" => tmp := x"0";      -- 0
        when x"31" => tmp := x"1";      -- 1
        when x"32" => tmp := x"2";      -- 2
        when x"33" => tmp := x"3";      -- 3
        when x"34" => tmp := x"4";      -- 4
        when x"35" => tmp := x"5";      -- 5
        when x"36" => tmp := x"6";      -- 6
        when x"37" => tmp := x"7";      -- 7
        when x"38" => tmp := x"8";      -- 8
        when x"39" => tmp := x"9";      -- 9
        when x"61" => tmp := x"a";      -- a
        when x"62" => tmp := x"b";      -- b
        when x"63" => tmp := x"c";      -- c
        when x"64" => tmp := x"d";      -- d
        when x"65" => tmp := x"e";      -- e
        when x"66" => tmp := x"f";      -- f
        when others => tmp := x"0";
    end case;
    return tmp;
end ascii2hex;

-- ASCII character constants
constant NUL : std_logic_vector (7 downto 0) := x"00";
constant CR  : std_logic_vector (7 downto 0) := x"0d";
constant BS  : std_logic_vector (7 downto 0) := x"08";

-- character buffer shift register file
constant iCHARBUF_DEPTH : integer := 4;          -- max = 16 characters deep
constant iCHARBUF_WIDTH : integer := 8;          -- character = 8 bits
type regfile_type is array(iCHARBUF_DEPTH-1 downto 0) of std_logic_vector(iCHARBUF_WIDTH-1 downto 0);
signal L_charBuf : regfile_type := (others => NUL); -- character buffer shift register file
signal L_charBuf_shift_en : std_logic := '0';      -- shift enable signal
signal L_charBuf_clr : std_logic := '0';          -- Clear character buffer
signal L_charBuf_isFull : std_logic := '0';        -- Character buffer is full

-- character buffer shift counter
signal L_charBuf_shift_ctr : integer range 0 to 4 := 0; -- shift counter

-- XRAM
constant iXRAM_ADDR_WIDTH : integer := 8;          -- width of instruction RAM address
```

```

constant iXRAM_DEPTH          : integer := 200;    -- depth of instruction RAM
signal L_XRAM_wr_addr         : unsigned(iXRAM_ADDR_WIDTH-1 downto 0) := (others=>'0'); --
signal L_XRAM_wr_ctr_en      : std_logic := '0';
signal L_XRAM_wr_ctr_clr     : std_logic := '0';

-- input register
signal L_rx_data_reg         : std_logic_vector (7 downto 0) := (others => '0');
signal L_CR_detected        : std_logic := '0';    -- input character = carriage return
signal L_BS_detected        : std_logic := '0';    -- input character = backspace
signal L_rx_data_ready      : std_logic := '0';    -- input data is ready
signal L_inst_reg_en        : std_logic := '0';

-- FSM state types
type state_type is (sIDLE, sWAIT, sSHIFT, sWRITE, sWRITE2, sERROR, sSETUP);
signal current_state, next_state: state_type;

begin

-- Register input character on RX_done_tick
input_reg: process(clk)
begin
    if rising_edge(clk) then
        if (I_rx_done_tick = '1') then
            L_rx_data_reg <= I_rx_data;
            L_rx_data_ready <= '1'; -- data ready flag
        else
            L_rx_data_ready <= '0'; -- data not ready
        end if;
    end if;
end process;
L_CR_detected <= '1' when L_rx_data_reg = CR else '0'; -- Async watchdog to detect CR
L_BS_detected <= '1' when L_rx_data_reg = BS else '0'; -- Async watchdog to detect CR

-- Shifts characters into the char buffer on the enable signal. Also contains shift counter
shift_reg: process(clk, L_charBuf_shift_en, L_charBuf_clr)
begin
    if rising_edge(clk) then
        if (L_charBuf_clr = '1') then
            L_charBuf <= (others => NUL); -- clear char buffer
            L_charBuf_shift_ctr <= 0;    -- clear shift counter
        elsif (L_charBuf_shift_en = '1') then
            L_charBuf(L_charBuf_shift_ctr) <= L_rx_data_reg; -- shift in character
            L_charBuf_shift_ctr <= L_charBuf_shift_ctr + 1; -- Shift count ++
        end if;
    end if;
end process;
L_charBuf_isFull <= '1' when L_charBuf_shift_ctr = 4 else '0'; -- ASYNC watchdog for full character buffer

output_reg: process(clk, L_inst_reg_en)
begin
    if rising_edge(clk) then
        if(L_inst_reg_en = '1') then
            Q_instruction_word <= ascii2hex(L_charBuf(0)) & ascii2hex(L_charBuf(1)) & ascii2hex(L_charBuf(2)) & ascii2hex(L_charBuf(3));
        end if;
    end if;
end process;

-- Counter for XRAM write address
write_counter: process(clk, L_XRAM_wr_ctr_clr, L_XRAM_wr_ctr_en)
begin
    if rising_edge(clk) then
        if (L_XRAM_wr_ctr_clr = '1') then
            L_XRAM_wr_addr <= to_unsigned(0, L_XRAM_wr_addr'length);
        elsif (L_XRAM_wr_ctr_en = '1') then
            L_XRAM_wr_addr <= L_XRAM_wr_addr + 1;
        end if;
    end if;
end process;
Q_X_addr <= std_logic_vector(L_XRAM_wr_addr);

-----
----- FSM CONTROLLER -----
-----
StateUpdate: process(clk)
begin
    if rising_edge(clk) then
        current_state <= next_state;
    end if;
end process;

StateMachine: process(current_state, L_rx_data_ready, L_CR_detected, I_program_en, L_BS_detected, L_charBuf_isFull)
begin
    -- Defaults
    L_XRAM_wr_ctr_clr <= '0';
    L_XRAM_wr_ctr_en <= '0';
    L_charBuf_shift_en <= '0';
    L_charBuf_clr <= '0';
    L_inst_reg_en <= '0';
    Q_X_wr_en <= '0';
    Q_error_start <= '0';
    next_state <= current_state;

```

```

case current_state is
  -- idle until set into programming mode
  when sIDLE =>
    L_charBuf_clr <= '1';
    if (I_program_en = '1') then
      next_state <= sSETUP;
    end if;

    -- Clear the XRAM write address
  when sSETUP =>
    L_XRAM_wr_ctr_clr <= '1';
    next_state <= sWAIT;

    -- wait for new character on rx_done_tick
  when sWAIT =>
    if (I_program_en = '0') then -- go to idle b/c execute mode begins
      next_state <= sIDLE;
    elsif (L_rx_data_ready = '1') then
      if (L_BS_detected = '1') then
        next_state <= sERROR;
      elsif (L_CR_detected = '1') then
        if (L_charBuf_isFull = '1') then
          next_state <= sWRITE;
        else
          next_state <= sERROR;
        end if;
      elsif (L_charBuf_isFull = '1') then
        next_state <= sERROR;
      else
        next_state <= sSHIFT;
      end if;
    end if;

    -- Shift received character into register file
  when sSHIFT =>
    L_charBuf_shift_en <= '1';
    next_state <= sWAIT;

    -- register instruction in output register
  when sWRITE =>
    L_inst_reg_en <= '1'; -- register instruction
    L_charBuf_clr <= '1'; -- clear character buffer now that command has been
    next_state <= sWRITE2;

    -- write contents of output register to XRAM
  when sWRITE2 =>
    Q_X_wr_en <= '1'; -- write output register to memory
    L_XRAM_wr_ctr_en <= '1'; -- increment write counter
    next_state <= sWAIT;

  when sERROR =>
    Q_error_start <= '1';
    L_charBuf_clr <= '1';
    next_state <= sWAIT;

  when others =>
    next_state <= sWAIT;

end case;
end process;

end Behavioral;

```

Error Generator

```
-- Class:          ENGS 128 15S
-- Engineer:       Brett Nicholas and Matt Metzler
--
-- Create Date:    05/27/2015 03:43:05 PM
-- Design Name:    Final Project
-- Module Name:    errorngen - Behavioral
-- Project Name:    MyRISC
-- Target Devices: Xilinx Arctix7 FPGA on Digilent BASYS3 project board
-- Tool Versions:  Xilinx Vivado
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity errorngen is
Port (
    clk           : in std_logic;
    I_error_start  : in std_logic;
    I_tx_done_tick : in std_logic;
    Q_tx_start     : out std_logic;
    Q_tx_data      : out std_logic_vector (7 downto 0));
end errorngen;

architecture Behavioral of errorngen is

    type string_type is array(0 to 5) of std_logic_vector(7 downto 0);
    signal L_string : string_type;

    type state_type is (sIDLE, sSTART, sWAIT, sCOUNT);
    signal current_state, next_state : state_type := sIDLE;

    --Counter signals
    signal L_count      : integer range 0 to 5;
    signal L_counter_inc : std_logic := '0';
    signal L_counter_clr : std_logic := '0';
    signal L_counter_full : std_logic := '0';

begin

--String Declarations
L_string(0) <= x"45";
L_string(1) <= x"52";
L_string(2) <= x"52";
L_string(3) <= x"4f";
L_string(4) <= x"52";
L_string(5) <= x"0d";

--Output Assignment
Q_tx_data <= L_string(L_count);

Counter: process(clk)
begin
    if rising_edge(clk) then
        if (L_counter_clr = '1') then
            L_count <= 0;
        elsif (L_counter_inc = '1') then
            L_count <= L_count + 1;
        end if;
    end if;
end process;
L_counter_full <= '1' when (L_count = 5) else '0';

StateUpdate: process(clk)
begin
    if rising_edge(clk) then
        current_state <= next_state;
    end if;
end process;

StateMachine: process(current_state, I_error_start, I_tx_done_tick, L_counter_full)
```

```

begin

    next_state <= current_state;
    Q_tx_start <= '0';
    L_counter_inc <= '0';
    L_counter_clr <= '0';

    case current_state is

        when sIDLE =>
            L_counter_clr <= '1';
            if I_error_start = '1' then
                next_state <= sSTART;
            end if;

        when sSTART =>
            Q_tx_start <= '1';
            next_state <= sWAIT;

        when sWAIT =>
            if (I_tx_done_tick = '1') then
                if (L_counter_full = '1') then
                    next_state <= sIDLE;
                else
                    next_state <= sCOUNT;
                end if;
            end if;

        when sCOUNT =>
            L_counter_inc <= '1';
            next_state <= sSTART;

        when others =>
            next_state <= sIDLE;

    end case;
end process;

end Behavioral;

```

Serial Receiver

```
-- Company:      Engs 31 09X
-- Engineer:     E.W. Hansen
--
-- Create Date:   18:29:23 07/19/2008
-- Design Name:
-- Module Name:   SerialRx - Behavioral
-- Project Name:  Lab 5
-- Target Devices: Spartan 3E / Nexys 2
-- Tool versions: Foundation ISE 11.2
-- Description:   Serial asynchronous receiver for Nexys 2 RS-232 port
--
-- Dependencies:
--
-- Revision:
-- Revision
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.all;
use ieee.math_real.all;

entity SerialRx is
  Port ( clk : in  STD_LOGIC;
        RsRx : in  STD_LOGIC;
        Q_rx_data : out STD_LOGIC_VECTOR (7 downto 0);
        Q_rx_done_tick : out STD_LOGIC );
end SerialRx;

architecture Behavioral of SerialRx is
  constant CLOCK_FREQUENCY : integer := 100000000; -- 100 MHz clock
  constant BAUD_RATE : integer := 115200; -- baud rate
  constant BAUD_RATE_COUNT : integer := CLOCK_FREQUENCY / BAUD_RATE; -- clocks per bit
  constant TICK_CTR_WIDTH : integer := integer(CEIL(LOG2(real(BAUD_RATE_COUNT))));

  signal rx_sync:      std_logic_vector(1 downto 0) := "11"; -- double synchronizer
  signal rx_bit:      std_logic; -- synchronized bit stream
  signal rx_reg:      std_logic_vector(9 downto 0) := (others=>'0'); -- start & data & stop

  signal tick_ctr:      unsigned(TICK_CTR_WIDTH-1 downto 0) := (others=>'0'); -- count clock ticks to find bits
  signal bit_ctr:      unsigned(3 downto 0) := x"0"; -- count received bits (0 to 10)
  signal rx_sample: std_logic;
  signal rx_shift: std_logic;
  signal rx_reg_full: std_logic;
  signal rx_output: std_logic;
  signal rx_init:      std_logic; -- load bit counter with 8 and reset shift counter

  type state_type is (s0, s1, s2, s3, s4);
  signal curr_state, next_state : state_type;

begin

Synchronizer: -- Double flop synchronizer
process(Clk)
begin
  if rising_edge(Clk) then
    rx_sync <= RsRx & rx_sync(1);
  end if;
end process Synchronizer;
rx_bit <= rx_sync(0); -- sync'd output is the lsb of the pair

TickCounter:
process(Clk)
begin
  if rising_edge(Clk) then
    rx_sample <= '0';
    if rx_init='1' then
      tick_ctr <= to_unsigned(BAUD_RATE_COUNT/2, TICK_CTR_WIDTH);
    elsif tick_ctr = 0 then
      rx_sample <= '1';
      tick_ctr <= to_unsigned(BAUD_RATE_COUNT, TICK_CTR_WIDTH);
    else
      tick_ctr <= tick_ctr-1;
    end if;
  end if;
end process TickCounter;

DataRegisters:
process(Clk)
```

```

begin
    if rising_edge(Clk) then
        if rx_shift='1' then          -- shift register
            rx_reg <= rx_bit & rx_reg(9 downto 1);
        end if;

        if rx_output='1' then         -- output register
            Q_rx_data <= rx_reg(8 downto 1);
        end if;
    end if;
end process DataRegisters;

BitCounter:
process(Clk, bit_ctr)
begin
    if rising_edge(Clk) then
        if rx_init = '1' then
            bit_ctr <= x"0";
        else
            if rx_shift='1' then
                bit_ctr <= bit_ctr+1;
            end if;
        end if;
    end if;

    rx_reg_full <= '0';
    if bit_ctr = "1010" then
        rx_reg_full <= '1';
    end if;
end process BitCounter;

RxControllerReg:
process(Clk)
begin
    if rising_edge(Clk) then
        curr_state <= next_state;
    end if;
end process RxControllerReg;

RxControllerComb:
process(rx_bit, rx_sample, rx_reg_full, curr_state)
begin
    -- defaults
    rx_init <= '0'; rx_shift <= '0';
    rx_output <= '0'; Q_rx_done_tick <= '0';
    next_state <= curr_state;
    --

    case curr_state is
        when s0 => rx_init <= '1';          -- wait for start bit
            if rx_bit = '0'
                then next_state <= s1;
            end if;

        when s1 =>
            if rx_reg_full='1'
                then next_state <= s3;          -- after 10 bits have been shifted
            elsif rx_sample='1'
                then next_state <= s2;          -- go to the output state
            end if;          -- go to the shift state

        when s2 => rx_shift <= '1';          -- shift the register
            next_state <= s1;

        when s3 => rx_output <= '1';          -- transfer to the output register
            next_state <= s4;

        when s4 => Q_rx_done_tick <= '1';    -- tell we're done
            next_state <= s0;

        when others =>
            next_state <= s0;
    end case;
end process RxControllerComb;

end Behavioral;

```

Serial Transmitter

```
-- Company:                      Engs 31 14X
-- Engineer:                     E.W. Hansen
--
-- Create Date:                  12:55:02 07/19/2008
-- Design Name:                  Lab 5
-- Module Name:                  SerialTx - Behavioral
-- Project Name:                 RS232
-- Target Devices:               Spartan 6 / Nexys 3
-- Tool versions:                Foundation ISE 14.4
-- Description:                  Serial asynchronous transmitter for Pmod RS-232 port
--
-- Revision:
-- Revision 0.01 - File Created
-- Rev (EWH) 7.17.2014, no external baud rate generator
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;
use ieee.math_real.all;

entity SerialTx is
    Port ( clk : in  STD_LOGIC;
          tx_data : in  STD_LOGIC_VECTOR (7 downto 0);
          tx_start : in  STD_LOGIC;
          tx : out  STD_LOGIC;
          tx_done_tick : out  STD_LOGIC);
end SerialTx;

architecture Behavioral of SerialTx is
    constant CLOCK_FREQUENCY : integer := 100000000;
    constant BAUD_RATE : integer := 115200;
    constant BAUD_COUNT : integer := CLOCK_FREQUENCY / BAUD_RATE;
    constant TICK_CTR_WIDTH : integer := integer(CEIL(LOG2(real(BAUD_COUNT))));

    signal br_cnt:                unsigned(TICK_CTR_WIDTH-1 downto 0) := (others=>'0'); -- baud rate counter

    -- 12 bits can handle 4800 baud at 10 MHz clock
    signal br_tick: std_logic;
    signal tx_reg: std_logic_vector(9 downto 0) := "1111111111"; -- 1 start bit, 8 data bits, 1 stop bit, no parity
    signal tx_ctr: unsigned(3 downto 0); -- count the bits that have been sent
    signal tx_load, tx_shift : std_logic; -- register control bits
    signal tx_empty: std_logic; -- register status bit
    type state_type is (sidle, ssync, sload, sshift, sdone, swait); -- state machine
    signal curr_state, next_state: state_type;

begin

BaudRateClock:
process(Clk)
begin
    if rising_edge(Clk) then
        if br_cnt = BAUD_COUNT-1 then
            br_cnt <= (others=>'0');
            br_tick <= '1';
        else
            br_cnt <= br_cnt+1;
            br_tick <= '0';
        end if;
    end if;
end process BaudRateClock;

DataRegister:
process( Clk )
begin
    if rising_edge( Clk ) then
        if (tx_load = '1') then
            tx_reg <= '1' & tx_data & '0'; -- load with stop & data & start
        elsif br_tick = '1' then
            tx_reg <= '1' & tx_reg(9 downto 1); -- the register is always shifting
        end if;
    end if;
end process DataRegister;
tx <= tx_reg(0); -- serial output port <= lsb

ShiftCounter:
process ( Clk )
begin
    if rising_edge( Clk ) then
        if (tx_load = '1') then
            tx_ctr <= x"A"; -- load counter with 10 when register is loaded
        elsif br_tick = '1' then
            if (tx_shift = '1') then
                if tx_ctr > 0 then
                    tx_ctr <= tx_ctr - 1;
                end if;
            end if;
        end if;
    end if;
end process;
end if;
```



```

        end if;
    end process ShiftCounter;
    tx_empty <= '1' when tx_ctr = x"0" else '0';

TxControllerComb:
process ( tx_start, tx_empty, br_tick, curr_state )
begin
    -- defaults
    next_state <= curr_state;
    tx_load <= '0'; tx_shift <= '0'; tx_done_tick <= '0';
    -- next state and output logic
    case curr_state is
        when sidle =>
            if tx_start = '1'
                then next_state <= ssync;
            end if;
            -- wait for start signal
        when ssync =>
            if br_tick = '1'
                then next_state <= sload;
            end if;
            -- sync up with baud rate
        when sload =>
            tx_load <= '1';
            next_state <= sshift;
            -- load the data register
        when sshift => tx_shift <= '1';
            if tx_empty = '1'
                then next_state <= sdone;
            end if;
            -- shift the bits out
            -- wait for shift counter
        when sdone => tx_done_tick <= '1';
            next_state <= swait;
            -- raise the done flag
        when swait =>
            if tx_start = '0'
                then next_state <= sidle;
            end if;
            -- wait for start signal to drop
        when others => next_state <= sidle;
    end case;
end process TxControllerComb;

TxControllerReg:
process ( Clk )
begin
    if rising_edge(Clk) then
        curr_state <= next_state;
    end if;
end process TxControllerReg;

end Behavioral;

```

Monopulser

```
-- Class:          ENGS 128 15S
-- Engineer:       Brett Nicholas and Matt Metzler
--
-- Create Date:    05/27/2015 03:43:05 PM
-- Design Name:    Final Project
-- Module Name:    Monopulser - Behavioral
-- Project Name:    MyRISC
-- Target Devices: Xilinx Arctix7 FPGA on Digilent BASYS3 project board
-- Tool Versions:  Xilinx Vivado
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity Monopulser is
Port ( clk          : in std_logic;
      button        : in std_logic;
      mono_out       : out std_logic);
end Monopulser;

architecture Behavioral of Monopulser is

    signal old_button    : std_logic := '0';
    signal new_button     : std_logic := '0';

begin

Registers: process(clk)
begin
    if rising_edge(clk) then
        old_button <= new_button;
        new_button <= button;
    end if;
end process;

mono_out <= '1' when (new_button = '1') and (old_button = '0') else '0';

end Behavioral;
```

Debouncer

```

LIBRARY eee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;

ENTITY debounce IS

    PORT(
        clk      : IN  STD_LOGIC; -- assumes 25Mhz clock
        button   : IN  STD_LOGIC; -- input signal to be debounced
        db_out    : OUT STD_LOGIC); -- debounced signal out
    END debounce;

ARCHITECTURE logic OF debounce IS
    constant NBITS : integer := 18; -- change this if too fast or too slow
    SIGNAL flipflops : STD_LOGIC_VECTOR(1 DOWNTO 0); --input flip flops (synchronizer)
    SIGNAL counter_set : STD_LOGIC; --sync reset to zero
    SIGNAL counter_out : STD_LOGIC_VECTOR(NBITS DOWNTO 0) := (OTHERS => '0');
    --counter size (19 bits gives approx 10ms delay with 25MHz clock)
    BEGIN

DFS: process(clk, flipflops) -- double flop synchronizer
begin
    IF rising_edge(clk) THEN
        flipflops <= button & flipflops(1);
    end if;
    counter_set <= flipflops(0) xor flipflops(1); -- determine when to start/reset counter
end process DFS;

-- Wait until the input has been stable (synchronizer holds "00" or "11" for
-- about 10 msec
DBtimer: PROCESS(clk)
BEGIN
    IF rising_edge(clk) THEN
        If(counter_set = '1') THEN -- reset counter because input is still bouncing
            counter_out <= (OTHERS => '0');
        ELSIF(counter_out(1) = '0') THEN -- use for simulation only
        ELSEIF(counter_out(NBITS) = '0') THEN -- use for implementation
            counter_out <= counter_out + 1;
        ELSE --stable input time is met
            db_out <= flipflops(1);
        END IF;
    END IF;
END PROCESS DBtimer;

END logic;

```

7-segment display

```
-- Company:      Engs 31 08X
-- Engineer:     E.W. Hansen
--
-- Create Date:   17:56:35 07/25/2008
-- Design Name:
-- Module Name:   mux7seg - Behavioral
-- Project Name:
-- Target Devices: Digilent Nexys 2 board
-- Tool versions:  Foundation ISE 10.1.01i
-- Description:    Multiplexed seven-segment decoder for the display on the
--                 Nexys 2 board
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

entity mux7seg is
    Port ( clk : in  STD_LOGIC;
          y0, y1, y2, y3 : in  STD_LOGIC_VECTOR (3 downto 0); -- digits
          seg : out  STD_LOGIC_VECTOR(0 to 6);                -- segments (a...g)
          an : out  STD_LOGIC_VECTOR (3 downto 0) );           -- anodes
end mux7seg;

architecture Behavioral of mux7seg is
    constant NCLKDIV: integer := 18;
    constant MAXCLKDIV: integer := 2*NCLKDIV-1; -- max count of clock divider
    signal cdcount: unsigned(NCLKDIV-1 downto 0) := (others => '0'); -- clock divider count
    signal CE : std_logic := '0'; -- clock enable
    signal adcount : unsigned(1 downto 0) := "00"; -- anode / mux selector count
    signal muxy : std_logic_vector(3 downto 0); -- mux output
    signal segh : std_logic_vector(0 to 6); -- segments (high true)
begin

-- Frequency of CE is Clock Frequency / 2^NCLKDIV = 100 MHz / 2^20, approx 95 Hz
ClockDivider: process(clk)
begin
    if rising_edge(clk) then
        if cdcount < MAXCLKDIV then
            cdcount <= cdcount+1;
            CE <= '0';
        else
            cdcount <= (others => '0');
            CE <= '1';
        end if;
    end if;
end process;

AnodeDriver: process(clk, adcount)
begin
    if rising_edge(clk) then
        if CE='1' then
            adcount <= adcount + 1;
        end if;
    end if;

    case adcount is
        when "00" => an <= "1110";
        when "01" => an <= "1101";
        when "10" => an <= "1011";
        when "11" => an <= "0111";
        when others => an <= "1111";
    end case;
end process AnodeDriver;

Multiplexer:
process(adcount, y0, y1, y2, y3)
begin
    case adcount is
        when "00" => muxy <= y0;
        when "01" => muxy <= y1;
        when "10" => muxy <= y2;
        when "11" => muxy <= y3;
        when others => muxy <= x"0";
    end case;
end process Multiplexer;

-- Seven segment decoder
with muxy select segh <=
```

```

"1111110" when x"0",
"0110000" when x"1",
"1101101" when x"2",
"1111001" when x"3",
"0110011" when x"4",
"1011011" when x"5",
"1011111" when x"6",
"1110000" when x"7",
"1111111" when x"8",
"1111011" when x"9",
"1110111" when x"a",
"0011111" when x"b",
"1001110" when x"c",
"0111101" when x"d",
"1001111" when x"e",
"0000111" when x"f",
"0000000" when others;
seg <= not(seg);

-- active-high definitions

-- Convert to active-low

end Behavioral;
```

Appendix C: Control Unit FSM Diagram

CONTROL UNIT FSM

